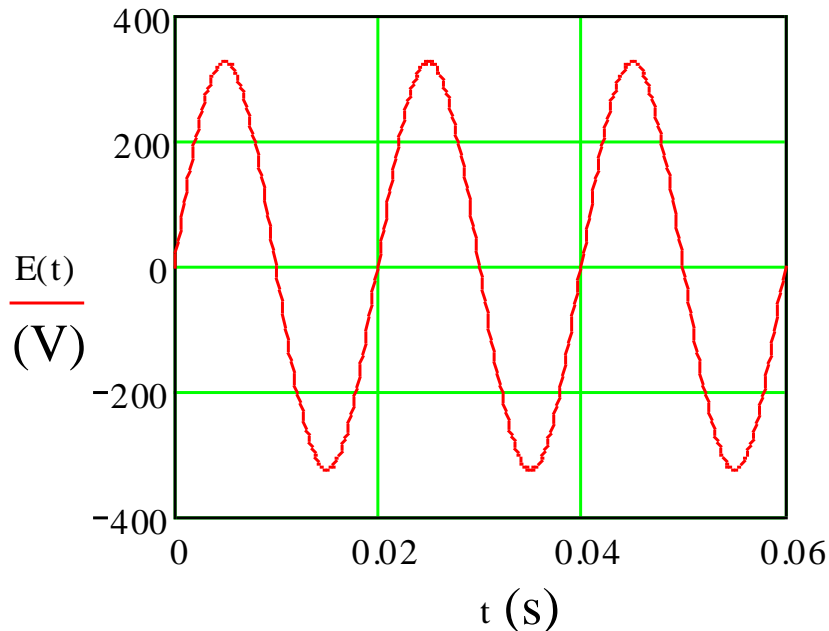


Lecture 19

- In this lecture we will look at:
 - ◆ Alternating current.
 - ◆ Resistive loads and phasors.
 - ◆ Capacitive loads and phasors.
 - ◆ Inductive loads and phasors.
- After this lecture, you should be able to answer the following questions:
 - Write down the equations which define the capacitive and inductive reactances. In what units are these measured?
 - Is the reactance of a capacitor largest for high or low frequencies?
 - Is the reactance of an inductor largest for high or low frequencies?
 - Describe the phase relationships between an AC voltage applied (separately) across a resistor, a capacitor and an inductance and the resulting current in each case.

Alternating Current


- Recall electricity generator, coil rotated in magnetic field.
- Freq. f_d , angular freq. $\omega_d = 2\pi f_d$.
- Get induced emf:
$$\mathcal{E}(t) = \mathcal{E}_m \sin \omega_d t \quad [19.1]$$
- E.g for mains, $\mathcal{E}_m = 325 \text{ V}$, $f_d = 50 \text{ Hz}$



- Need to understand behaviour of electrical devices when driven by emf varying sinusoidally with time.
- This emf will induce current in electrical components.
- Label amplitude of current I .
- May be out of phase with emf, so write $i = I \sin(\omega_d t - \phi)$, allowing for phase shift of ϕ w.r.t. driving voltage.
- Consider separately effects of resistive, capacitive and inductive loads.

Resistive Load

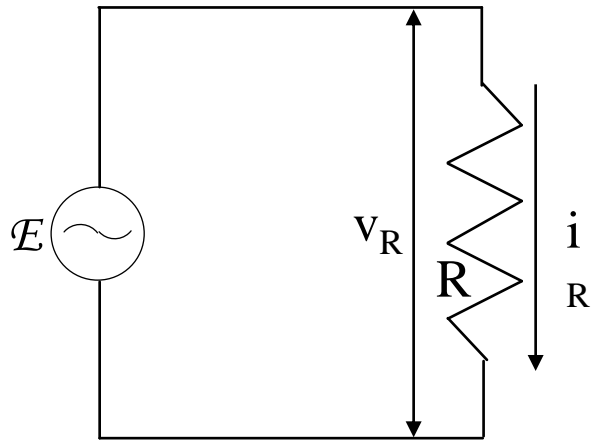- Circuit consists of alternating emf and resistance:



- Using Kirchoff's loop rule, we have:
 $\mathcal{E} - v_R = 0$.
- Inserting the expression for the emf we have $v_R = \mathcal{E}_m \sin \omega_d t$ or, using V_R to represent the amplitude of the potential across R , $v_R = V_R \sin \omega_d t$.


- The current through the resistor is given by $i = v/R$, therefore:

$$i_R = \frac{V_R}{R} \sin \omega_d t \quad [19.2]$$

- We can write this as $i_R = I_R \sin \omega_d t$.
- The amplitudes of the current and voltage are related by:
 $V_R = I_R R \quad [19.3]$
- The phase shift $\phi = 0$: the voltage across the resistor and the current through it are in phase.
- These relationships apply for all resistors in AC circuits.

Resistive Loads and Phasors

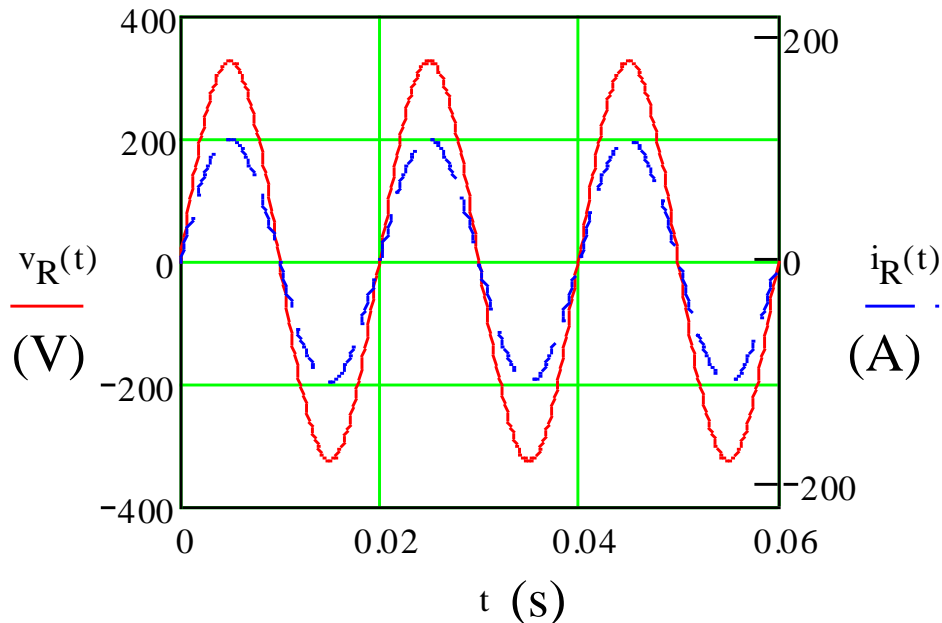- Plotting the voltage across the resistor and the current through it (using $\mathcal{E}_m = 325 \text{ V}$ and $R = 3 \ \Omega$):




- See the voltage and the current oscillate together, i.e. are in phase.


- The voltage and current can also be represented as phasors.
- Phasors are vectors whose length represents the magnitude of the voltage or current.
- The projection of the phasor on the vertical axis represents the voltage or current at a particular time.
- The phasors rotate in a positive direction (i.e. anticlockwise) around the origin with angular velocity ω_d .

Resistive Loads and Phasors

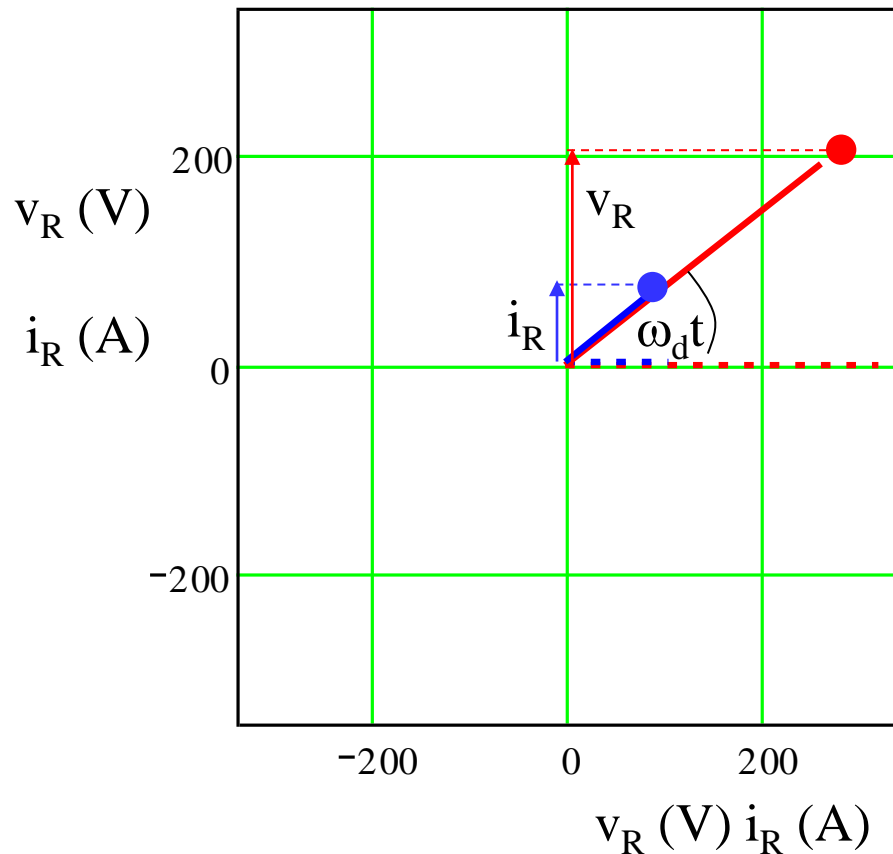- Static picture phasors for voltage across, and current through, resistor (parameters as before) at time t :




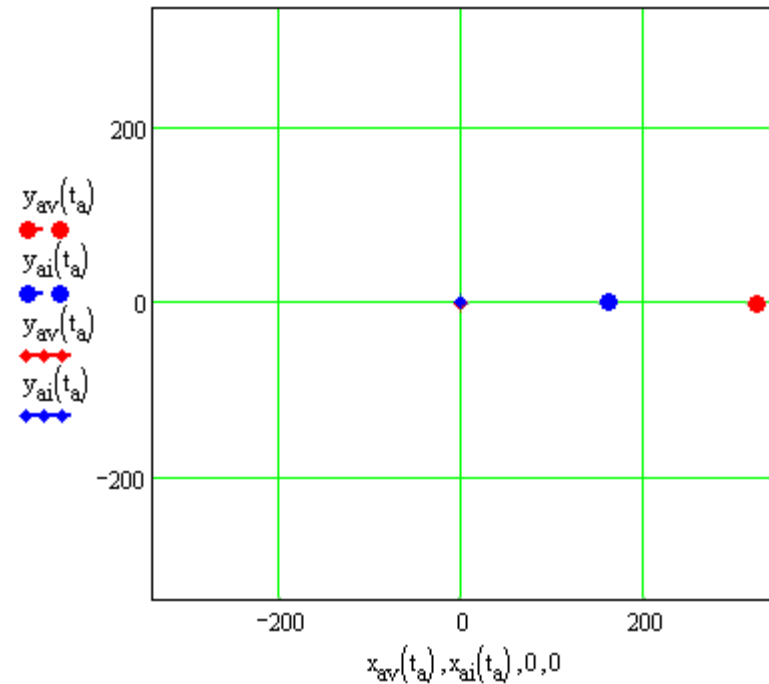- Allowing the phasors to rotate, we see how they describe the time variation of the current and voltage:



Capacitive Load

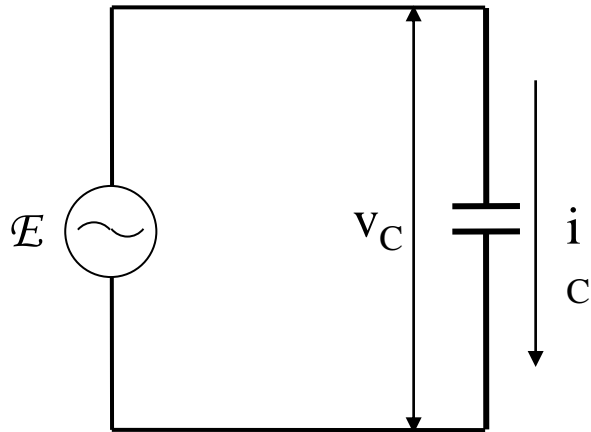- Circuit consists of alternating emf and capacitance:




- Using Kirchoff's loop rule, we have:
 $\mathcal{E} - v_C = 0.$
- Inserting the expression for the emf we have:
 $v_C = \mathcal{E}_m \sin \omega_d t$ or
 $v_C = V_C \sin \omega_d t$ [19.4]

- From the definition of capacitance:
 $q_C = C v_C = C V_C \sin \omega_d t.$
- From this we can find the current:
 $i_C = \frac{dq_C}{dt} = \omega_d C V_C \cos \omega_d t.$
- Introduce the capacitive reactance:
 $X_C = \frac{1}{\omega_d C}$ (unit Ω) [19.5]
- Using the substitution $\cos \theta = \sin \left(\theta + \frac{\pi}{2} \right)$ the expression for i_C becomes:
 $i_C = \frac{V_C}{X_C} \sin \left(\omega_d t + \frac{\pi}{2} \right).$
- Writing this in our standard form,
 $i_C = I_C \sin (\omega_d t - \phi)$
with $\phi = -\pi/2$ and $V_C = I_C X_C$ [19.6]


Phasors for Capacitive Loads

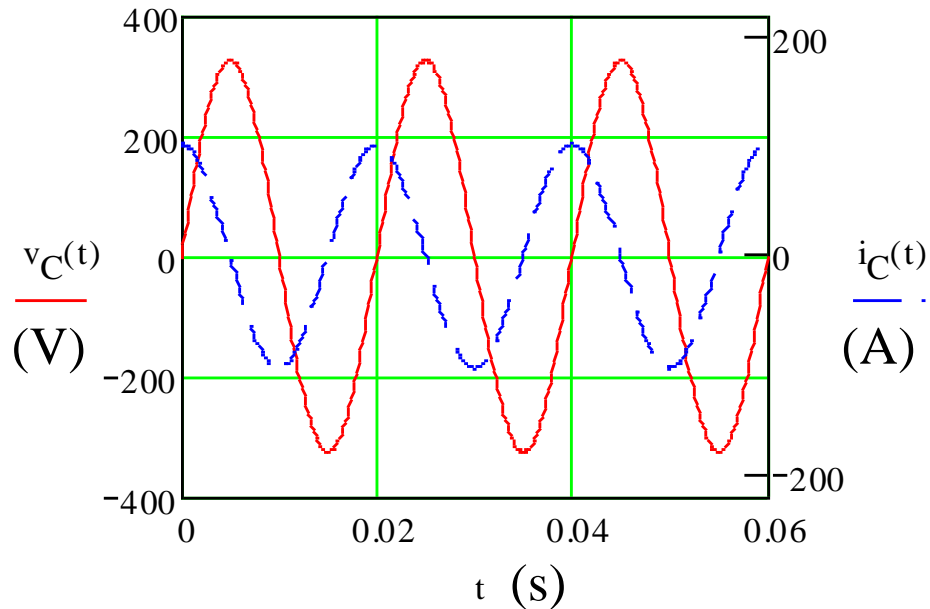- Plotting the voltage across the inductor and the current through it (using $\mathcal{E}_m = 325 \text{ V}$ and $C = 1 \text{ mF}$):




- We see the current leads the voltage by $\pi/2$, (i.e. current reaches peak before voltage).

- In terms of phasors, static picture:

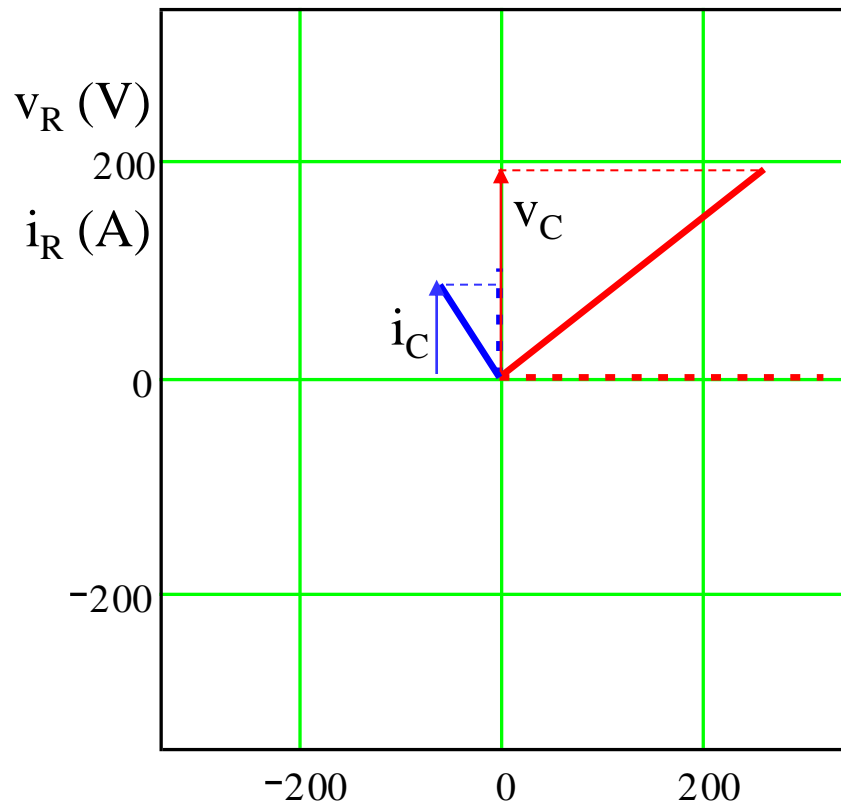


Phasors for Capacitive Loads

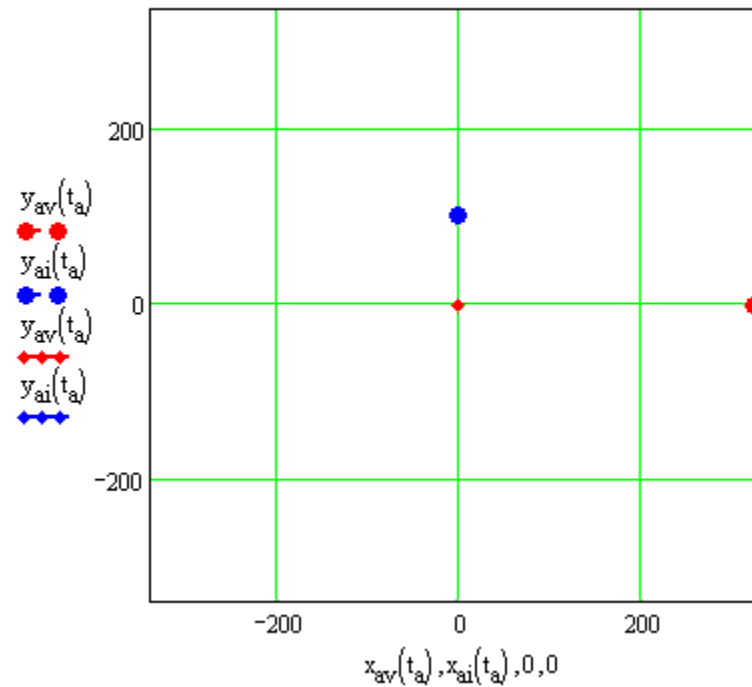- Animation of phasors for capacitive loads:



Inductive Load

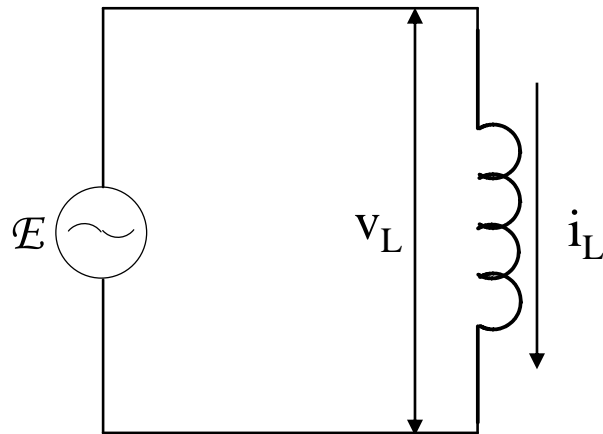- Circuit consists of alternating emf and inductance:



- Using Kirchoff's loop rule, we have:

$$\mathcal{E} - v_L = 0.$$

- Inserting the expression for the emf we have:

$$v_L = \mathcal{E}_m \sin \omega_d t \text{ or}$$

$$v_L = V_L \sin \omega_d t \quad [19.7]$$

- From the definition of inductance:

$$v_L = L \frac{di_L}{dt}.$$

- We thus have: $\frac{di_L}{dt} = \frac{V_L}{L} \sin \omega_d t$.

- $i_L = \int \frac{di_L}{dt} dt = \frac{V_L}{L} \int \sin \omega_d t dt = -\frac{V_L}{\omega_d L} \cos \omega_d t$.

- Introduce the inductive reactance:

$$X_L = \omega_d L \text{ (units } \Omega) \quad [18.8]$$

- Using the substitution $-\cos \theta = \sin(\theta - \frac{\pi}{2})$ the expression for i_L becomes:

$$i_L = \frac{V_L}{X_L} \sin\left(\omega_d t - \frac{\pi}{2}\right).$$


- Writing this in our standard form,

$$i_L = I_L \sin(\omega_d t - \phi)$$

$$\text{with } \phi = \pi/2 \text{ and } V_L = I_L X_L \quad [19.9]$$

Inductive Loads and Phasors

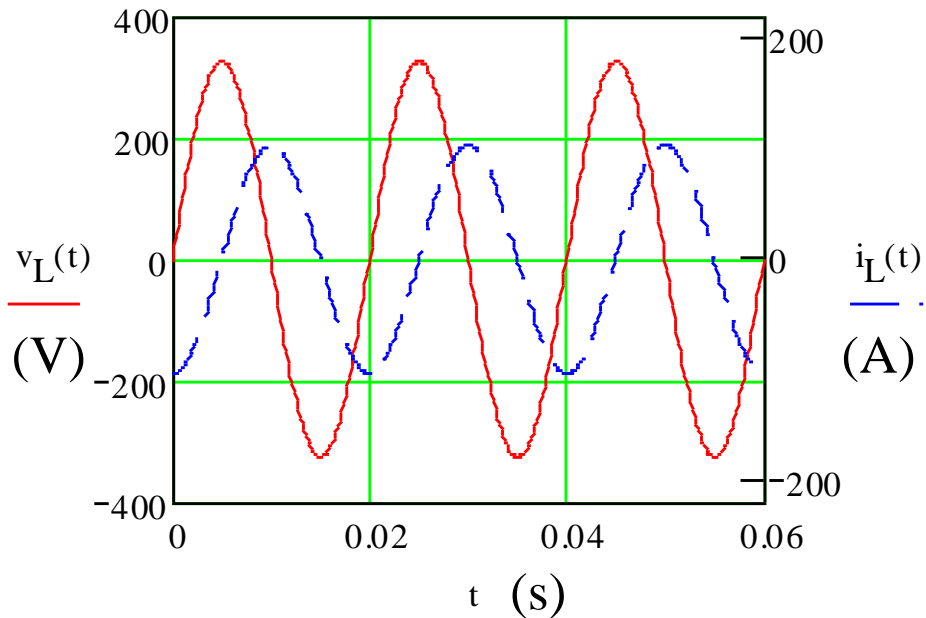- Plotting the voltage across the resistor and the current through it (using $\mathcal{E} = 325 \text{ V}$ and $L = 10 \text{ mH}$):



- We see the current lags the voltage by $\pi/2$, (i.e. current reaches peak after voltage).

- In terms of phasors, static picture:

