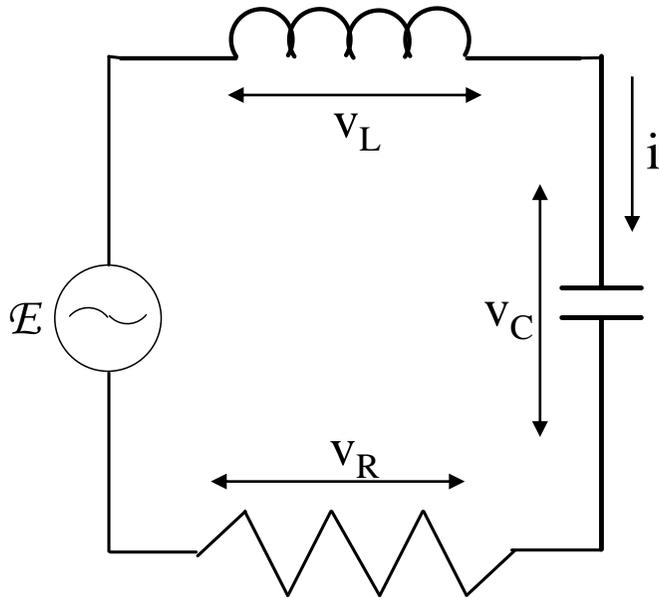


Lecture 20

- In this lecture we will look at:
 - ◆ Series LCR circuit.
 - ◆ Resonance.
 - ◆ Transients.
 - ◆ Power in AC circuits.
- After this lecture, you should be able to answer the following questions:
 - What is the impedance of a resistance R , an inductance L and a capacitance C connected in series?
 - Describe how the capacitive and inductive reactances change as the frequency of the sinusoidal signal driving a series LCR circuit increases from well below the circuit's resonant frequency to well above it.
 - Explain the difference between the amplitude of an AC current and the rms value of the current. Why is the rms value a useful quantity?


Series LCR Circuit

- Have looked at AC circuits containing L, C and R separately.
- What happens when all are present, connected in series?




- Same current flows through all components.

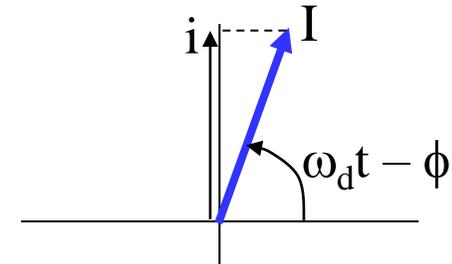- Draw phasors for circuit, first current, $i = I \sin(\omega_d t - \phi)$:




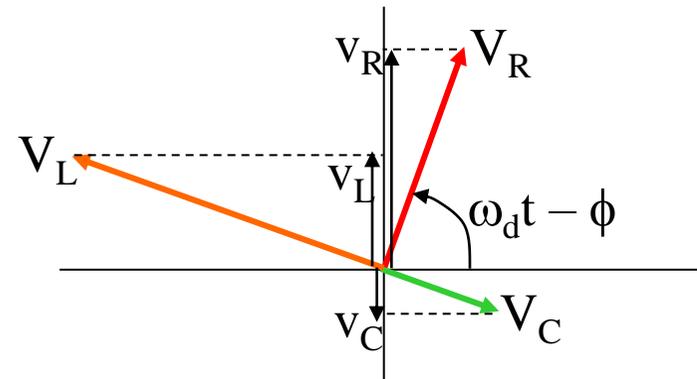- Now phasors for v_R , v_C and v_L , with the phase relationships: i same as v_R ; i leads v_C by $\pi/2$; i lags v_L by $\pi/2$.




Series LCR Circuit

- Phasor for emf:

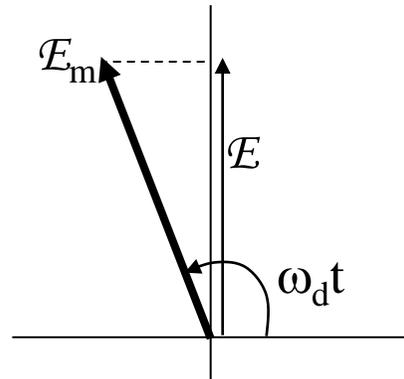

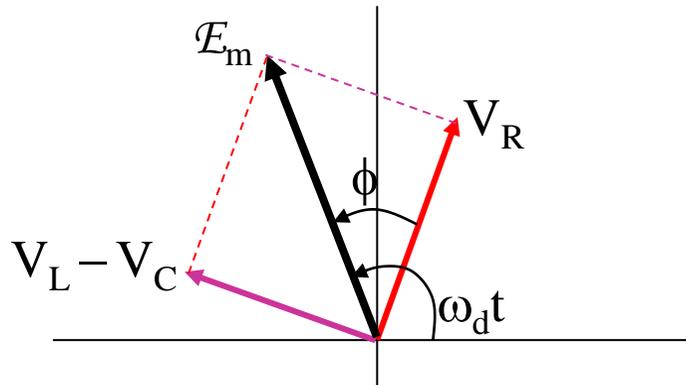- From the loop rule $\mathcal{E} = v_R + v_C + v_L$.
- Hence sum of phasors for v_L , v_C and v_R must give phasor for emf:



- Phasors for v_L and v_C have opposite directions, so mag. of sum is $V_L - V_C$.

- From Pythagoras' theorem,

$$\mathcal{E}_m^2 = V_R^2 + (V_L - V_C)^2.$$

- Remember $V_R = IR$, $V_C = IX_C$ and $V_L = IX_L$, so:

$$\mathcal{E}_m^2 = (IR)^2 + (IX_L - IX_C)^2.$$

- Rearranging allows us to determine the amplitude of the current:


$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{\mathcal{E}_m}{Z} \quad [20.1]$$

- Here we have defined the impedance:

$$\begin{aligned} Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2} \end{aligned} \quad [20.2]$$


Series LCR Circuit

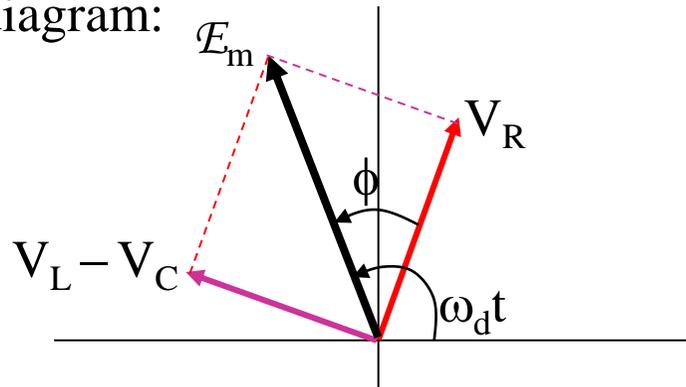- What about the relative phase of the current and the voltage?
- Look again at the LCR phasor diagram:




- We see $\tan \phi = \frac{V_L - V_C}{V_R}$
 $= \frac{IX_L - IX_C}{IR}$
 $= \frac{X_L - X_C}{R}$ [20.3]

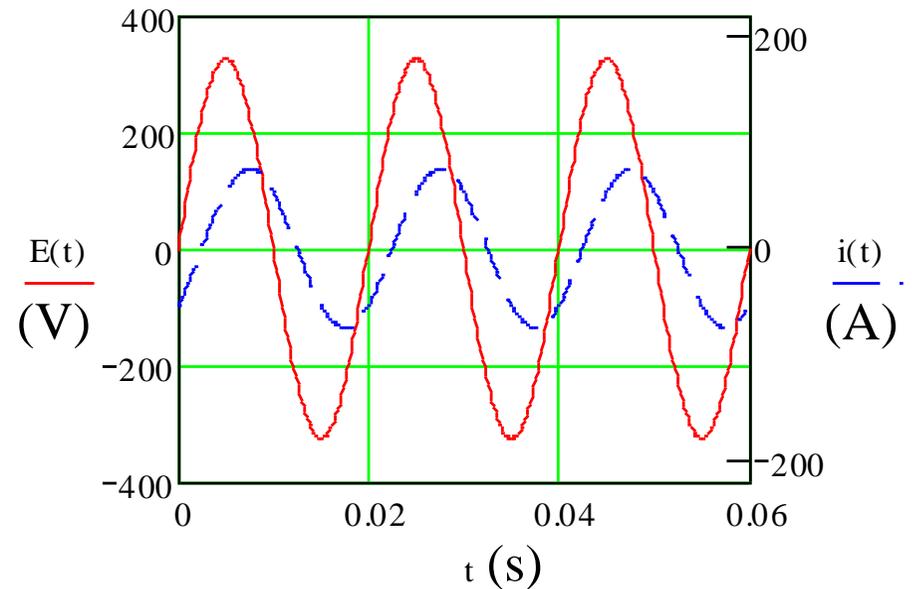- Now look at some LCR circuits.
- All with $\mathcal{E}_m = 325 \text{ V}$, $f = 50 \text{ Hz}$:
- $R = 3\Omega$, $C = 100 \text{ mF}$, $L = 10 \text{ mH}$ so $X_C = 0.032 \Omega$ and $X_L = 3.14 \Omega$.




Series LCR Circuit

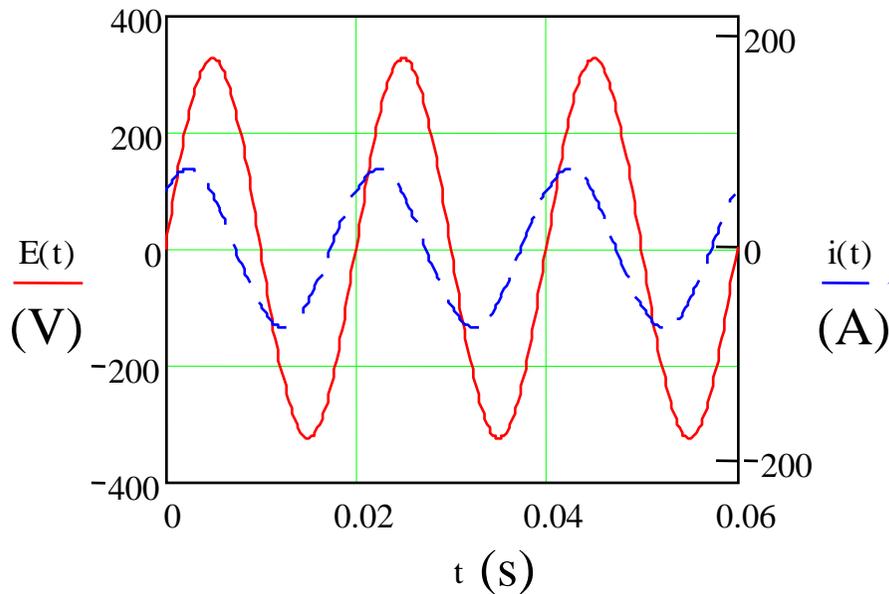- $R = 3\Omega$, $C = 1 \text{ mF}$, $L = 0.1 \text{ mH}$ so $X_C = 3.18 \Omega$ and $X_L = 0.031 \Omega$.



- $X_L > X_C$, more inductive than capacitive, ϕ +ive, i lags v .
- $X_C > X_L$, more capacitive than inductive, ϕ -ive, i leads v .

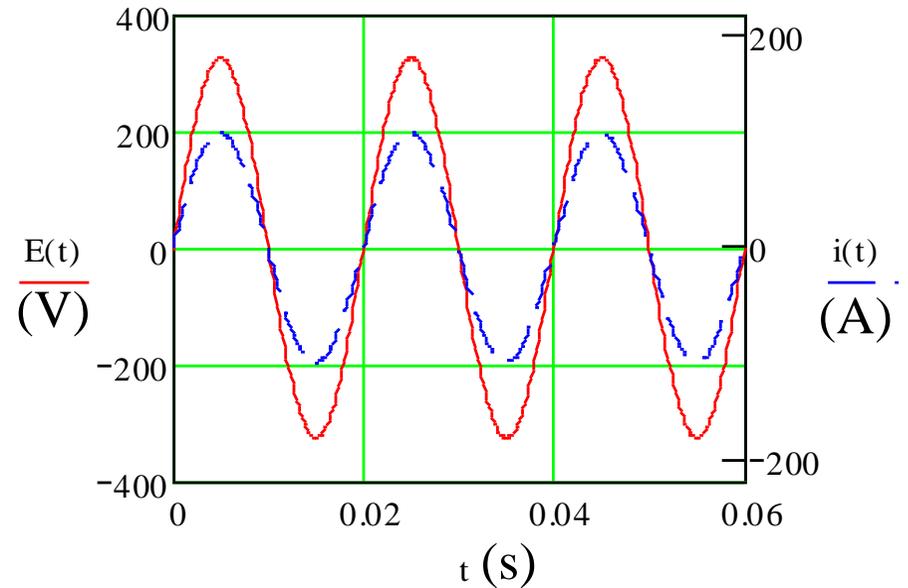- $R = 3$, $C = 1 \text{ mF}$, $L = 10 \text{ mH}$ so $X_C = 3.18 \Omega$ and $X_L = 3.14 \Omega$.



- $X_L \approx X_C$.
- Notice current large and $\phi \approx 0$.

Series LCR Circuit: Resonance

- Remember:

$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}.$$

- Resonance (maximum amplitude of current) when:

$$X_L = X_C \quad [20.4]$$

- Recall also:

$$\tan \phi = \frac{X_L - X_C}{R}.$$

- See $\tan \phi = 0$, and hence $\phi = 0$, when $X_L = X_C$.

- Can also change relationship between capacitive and inductive reactances by changing frequency at which circuit is driven.

- Current amplitude given by:

$$I = \frac{\mathcal{E}_m}{Z} = \frac{\mathcal{E}_m}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}.$$

- Maximum when:

$$\omega_d L - \frac{1}{\omega_d C} = 0 \Rightarrow \omega_d = \frac{1}{\sqrt{LC}} \quad [20.5]$$


- Recall natural frequency of LCR circuit is:

$$\omega' = \sqrt{\omega^2 - (R/2L)^2} \approx \omega$$

$$\text{where } \omega = 1/\sqrt{LC}$$


Resonance and Phase

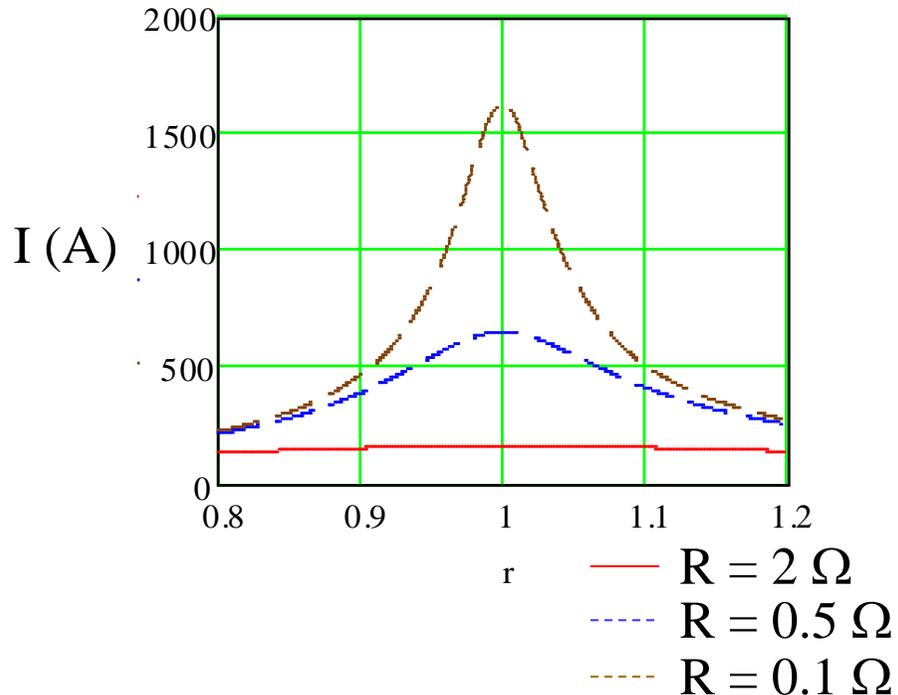- Plot current amplitude as function of $r = \omega_d/\omega$, for $R = 2, 0.5$ and 0.1Ω :



- Maximum always when $\omega_d \approx \omega$, but sharpness of resonance changes.

- Phase also change as frequency varies:

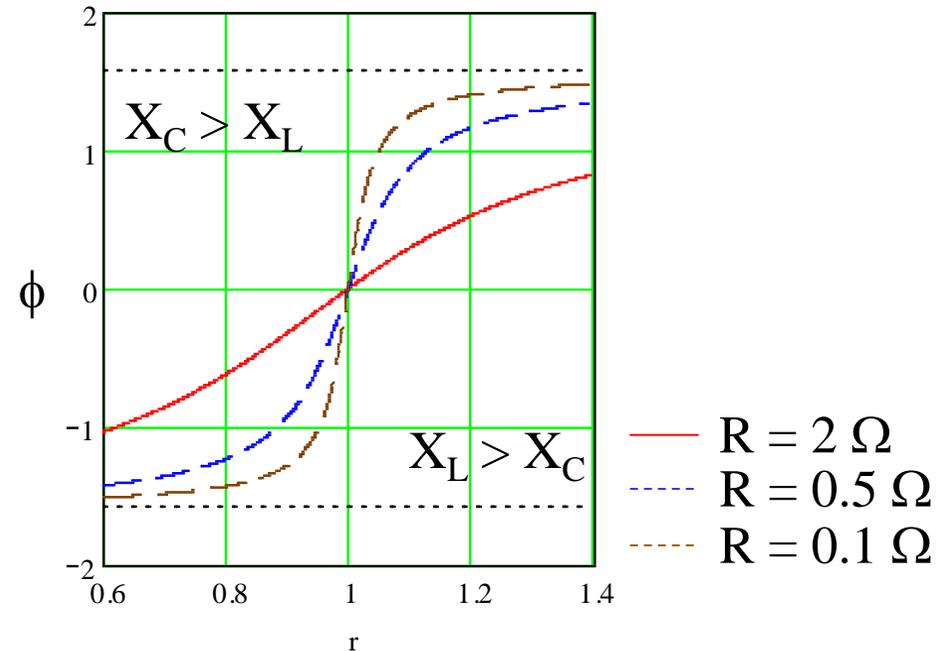


- Phase increases from $-\pi/2$, through zero as frequency passes through resonance, to $+\pi/2$.

Transients

- Note, when the emf is first applied, it can take some time for the current to settle down to the steady state described by the equation $i = I \sin(\omega_d t - \phi)$.
- The additional current that flows initially is called the transient current.
- The speed with which the transient current dies out is determined by the time constants of the circuit $\tau = L/R$ and $\tau = RC$.

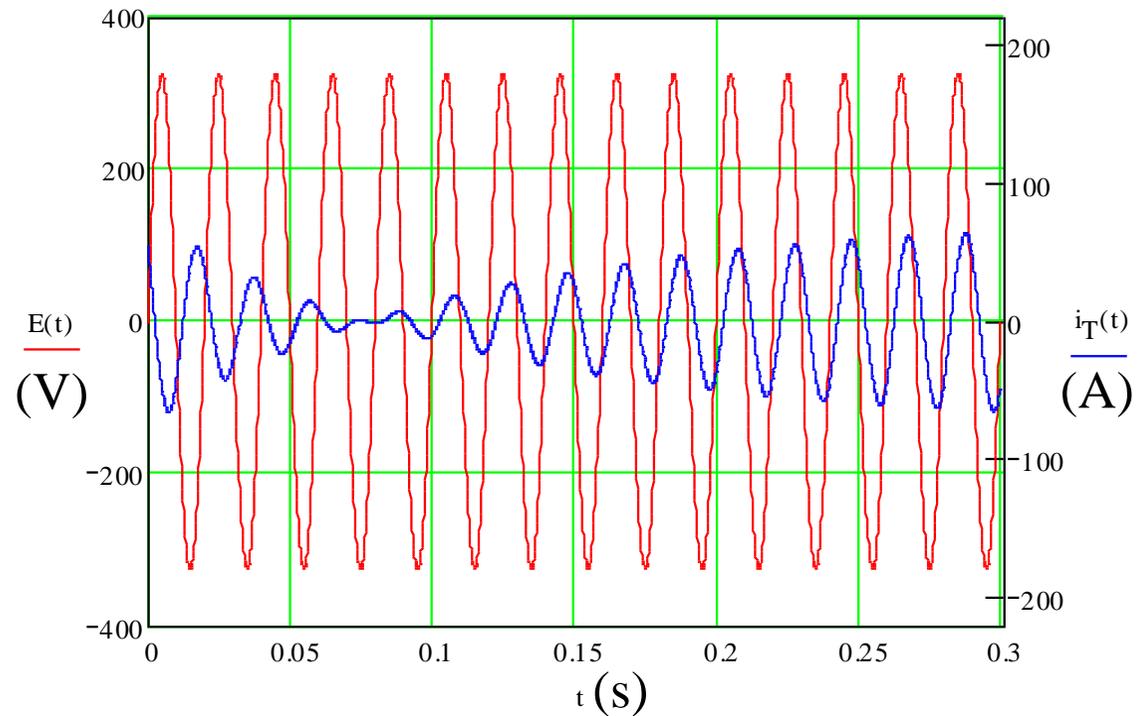- Example of behaviour that might be observed in LCR circuit at “start-up”:




Power in AC Circuits

- In LCR circuit energy is shifted between C and L (i.e. E and B fields) and lost to the circuit through the R.
- If have emf, this replaces energy lost through R.
- Power dissipated in R given by:
 $P = i^2 R = I^2 \sin^2(\omega_d t - \phi) R.$
- Mean rate of energy loss is this averaged over time.
- From plot opposite, see average value of $\sin^2 \theta$, $\langle \sin^2 \theta \rangle = 1/2$, so:

$$P_{\text{avg}} = I^2 R \langle \sin^2(\omega_d t - \phi) \rangle$$
$$= \frac{I^2 R}{2} \quad [20.6]$$

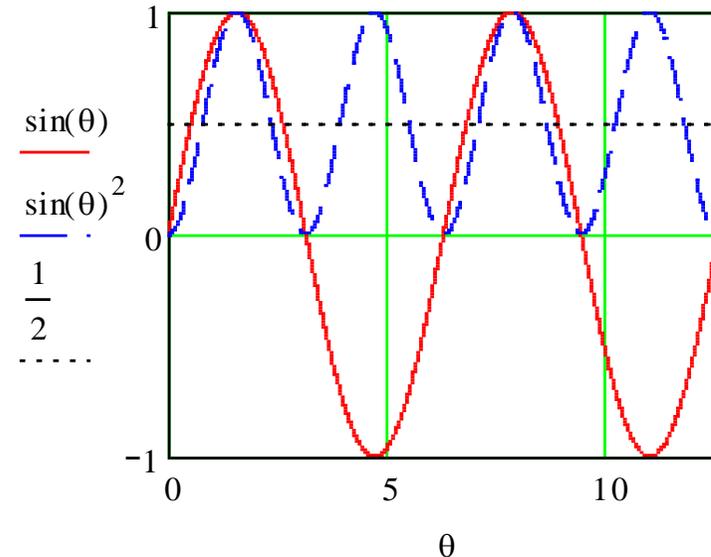- Plot of $\sin \theta$ and $\sin^2 \theta$:



- Introducing the quantity

$$I_{\text{rms}} = I/\sqrt{2} \quad [20.7]$$

we can write:

$$P_{\text{avg}} = I_{\text{rms}}^2 R \quad [20.8]$$

Power in AC Circuits

- Similarly define $V_{\text{rms}} = V/\sqrt{2}$ [20.9]
and $\mathcal{E}_{\text{rms}} = \mathcal{E}_m/\sqrt{2}$ [20.10]

- Remember we have:

$$I = \frac{\mathcal{E}_m}{Z} = \frac{\mathcal{E}_m}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}.$$

- We can divide through by $\sqrt{2}$ to get:

$$\frac{I}{\sqrt{2}} = \frac{\mathcal{E}_m/\sqrt{2}}{Z} = \frac{\mathcal{E}_m/\sqrt{2}}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}.$$


- So we can write:

$$I_{\text{rms}} = \frac{\mathcal{E}_{\text{rms}}}{Z} = \frac{\mathcal{E}_{\text{rms}}}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}.$$

- Using this we can recast the expression for the average power:

$$\begin{aligned} P_{\text{avg}} &= I_{\text{rms}}^2 R = \frac{\mathcal{E}_{\text{rms}}}{Z} I_{\text{rms}} R \\ &= \mathcal{E}_{\text{rms}} I_{\text{rms}} \frac{R}{Z}. \end{aligned}$$

- But, recall:

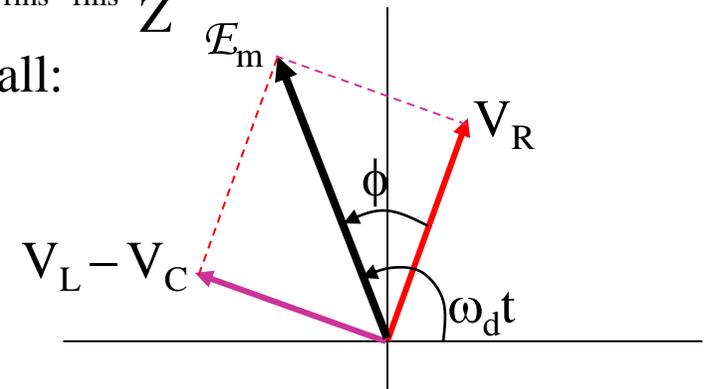

- So $\cos \phi = \frac{V_R}{\mathcal{E}_m} = \frac{IR}{IZ} = \frac{R}{Z}$ [20.11]

- Hence $P_{\text{avg}} = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi$ [20.12]