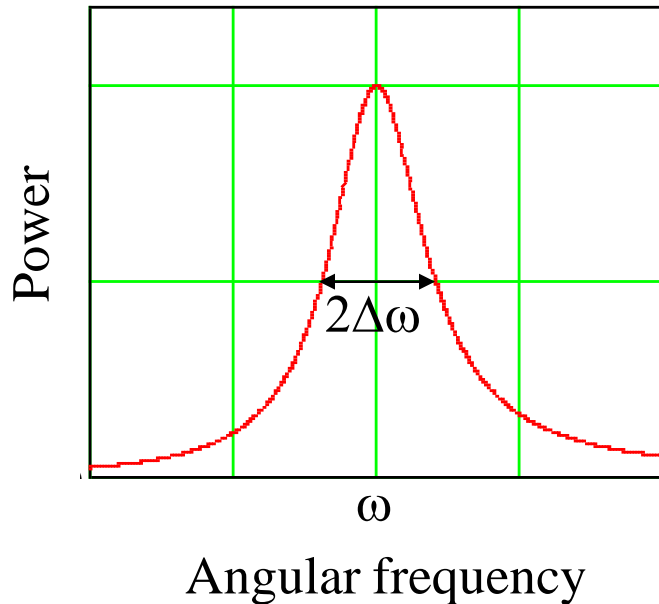


Lecture 21

- In this lecture we will look at:
 - ◆ Power and resonance.
 - ◆ The quality factor of a circuit.
 - ◆ Describing AC circuits using complex numbers.
- After this lecture, you should be able to answer the following questions:
 - Describe how the power dissipated in a series LCR circuit varies with the frequency of the signal driving the circuit.
 - How is the Q value of a circuit related to the width of the peak in the power spectrum at resonance?
 - How would you ensure that a series LCR circuit had a large Q value?

Power and Resonance

- Average power maximum when $\cos \phi = 1$, i.e. $\phi = 0$, the resonance condition.
- Look at power as function of frequency:



- Full width (of peak at) half maximum (power) $\text{FWHM} = 2\Delta\omega$.
- Define the quality factor (the sharpness of the resonance):

$$Q = \frac{\omega}{2\Delta\omega} \quad [21.1]$$

- Now:

$$P_{\text{rms}} = I_{\text{rms}}^2 R = \frac{\mathcal{E}_{\text{rms}}^2 R}{R^2 + (\omega_d L - 1/\omega_d C)^2}$$

$$P_{\text{peak}} = \frac{\mathcal{E}_{\text{rms}}^2 R}{R^2} = \frac{\mathcal{E}_{\text{rms}}^2}{R}$$

- To work out width, need ω_d at which power has decreased to $P_{\text{peak}}/2$:

$$\frac{P_{\text{rms}}}{P_{\text{peak}}} = \frac{\mathcal{E}_{\text{rms}}^2 R}{R^2 + (\omega_d L - 1/\omega_d C)^2} \times \frac{R}{\mathcal{E}_{\text{rms}}^2} = \frac{1}{2}$$

Power and Resonance: Quality factor of Circuit

- From this we get:

$$\frac{R^2}{R^2 + (\omega_d L - 1/\omega_d C)^2} = \frac{1}{2}$$

$$\Rightarrow R^2 = (\omega_d L - 1/\omega_d C)^2$$

$$\text{or } \omega_d L - 1/\omega_d C = \pm R$$

- This can be written as a quadratic equation in ω_d :

$$L\omega_d^2 \mp R\omega_d - 1/C = 0$$

$$\Rightarrow \omega_d = \frac{\pm R \pm \sqrt{R^2 + 4L/C}}{2L}.$$

- Only +ive solutions of this make sense (can't have -ive frequency!) so discard the two solutions with the second minus sign.

- The remaining +ive solutions must represent the $\omega + \Delta\omega$ and $\omega - \Delta\omega$.

- Subtracting these gives:

$$2\Delta\omega = \frac{+R + \sqrt{R^2 + 4L/C}}{2L} - \frac{-R + \sqrt{R^2 + 4L/C}}{2L}$$
$$= R/L.$$

- Hence:

$$Q = \frac{\omega}{2\Delta\omega} = \frac{\omega}{R/L}, \text{ so } Q = \frac{\omega L}{R} \quad [21.2]$$

- At resonance, $\omega L = 1/\omega C$, so we can also write this:

$$Q = \frac{1/\omega C}{R} = \frac{1}{\omega C R} \quad [21.3]$$

- We see small R relative to X_L or X_C means large Q or sharp resonance.

Quality Factor of Circuit and Energy Loss

- There is a second definition of the quality factor of a circuit:

$$Q = 2\pi \frac{\text{energy stored}}{\text{energy lost per cycle}}$$
$$= \frac{\text{energy stored}}{\text{energy lost per radian}}.$$

- The energy stored (e.g. when it is all in the inductance) is:

$$E_{\text{stored}} = \frac{1}{2} LI^2.$$

- The energy lost per cycle is:

$$E_{\text{lost}} = P_{\text{avg}} T = \frac{I^2 R}{2} T = \frac{I^2 R}{2} \frac{2\pi}{\omega}.$$

- Hence:


$$Q = 2\pi \frac{\frac{1}{2} LI^2}{I^2 R / 2 \times 2\pi / \omega}, \text{ or } Q = \frac{\omega L}{R}.$$

- The two definitions lead to the same mathematical expression.
- A circuit with a large Q value is thus one for which the resonance is sharp, but also one for which the energy lost per cycle is a small proportion of the stored energy.
- This is the end of the course!

Complex Numbers

- An alternative formalism for describing AC circuits is offered by complex numbers.
- A complex number can be written:
 $\mathbf{z} = x + jy$.
- The real part of \mathbf{z} is x , that is:
 $\text{Re}(\mathbf{z}) = x$.
- The imaginary part of \mathbf{z} is y , that is:
 $\text{Im}(\mathbf{z}) = y$.
- The quantity j is defined by:
 $j^2 = -1$ or $j = \sqrt{-1}$.
- A point in the complex plane can be used to represent \mathbf{z} (in the Argand diagram).

- Argand diagram:

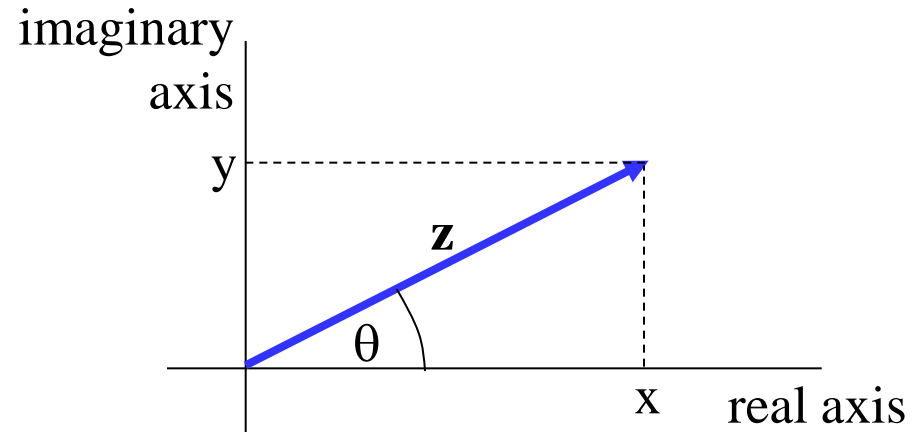

- De Moivre's theorem states:

$$\exp[j\theta] = \cos \theta + j \sin \theta$$

$$\Rightarrow \cos \theta = \text{Re}(\exp[j\theta])$$


$$\text{and } \sin \theta = \text{Im}(\exp[j\theta]).$$

- Hence $\mathbf{z} = z \exp [j\theta]$, where:

$$z = |\mathbf{z}| = \sqrt{x^2 + y^2} \quad \text{and} \quad \theta = \tan^{-1} \left[\frac{y}{x} \right].$$

Complex Numbers and AC Circuits

- Can represent quantities in AC circuits, e.g. emf $\mathcal{E} = \mathcal{E}_m \sin(\omega_d t)$, using:
 - ◆ Phasors, vector length \mathcal{E}_m rotating at angular frequency ω .
 - ◆ Complex number, $\mathcal{E} = \mathcal{E}_m \exp[j\omega_d t]$.
- Choosing the imaginary part of \mathcal{E} would give for the emf:
 $\mathcal{E} = \text{Im}(\mathcal{E}) = \mathcal{E}_m \sin(\omega_d t)$.
- Choosing the real part gives:
 $\mathcal{E} = \text{Re}(\mathcal{E}) = \mathcal{E}_m \cos(\omega_d t)$.
- Usually, the real part is used to represent the emf driving a circuit: in the rest of this lecture, $\mathcal{E} = \mathcal{E}_m \cos(\omega_d t)$.
- Complex numbers allow a compact and convenient description of AC circuits.
- Consider our series LCR circuit:

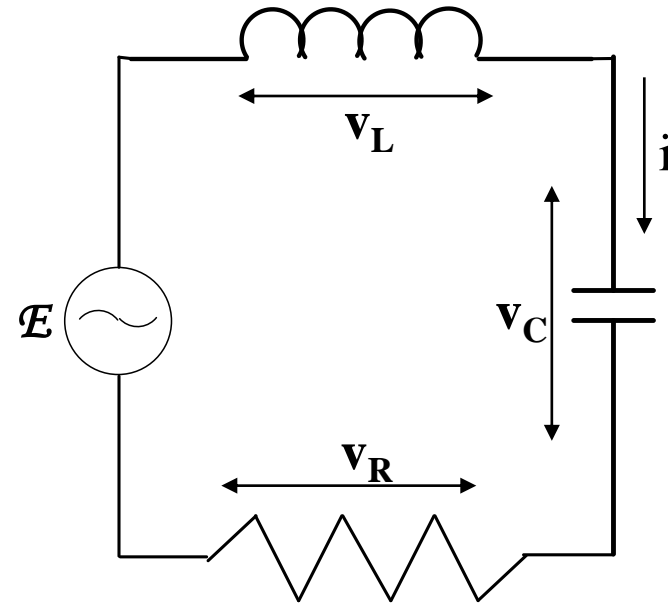

- Kirchoff's loop rule tells us:
 $\mathcal{E} = v_R + v_C + v_L$.

Complex Numbers and AC Circuits

- Using the familiar expressions for the voltage across the capacitance and the inductance:

$$\mathcal{E} - L \frac{di}{dt} - \frac{1}{C} \int i dt = iR.$$

- We are representing i as a complex number as it must also be sinusoidal.
- We must also allow the phase of i to be different to that of v , so we write:
 $i = I \exp[j(\omega_d t - \phi)].$
- Differentiating and integrating i we

have:

$$\frac{di}{dt} = j\omega_d I \exp[j(\omega_d t - \phi)] \text{ and}$$

$$\int i dt = \frac{1}{j\omega_d} I \exp[j(\omega_d t - \phi)].$$

- Substituting these expressions into our integro-differential equation:

$$\mathcal{E}_m \exp[j\omega_d t] - j\omega_d L I \exp[j(\omega_d t - \phi)] - \frac{1}{j\omega_d C} I \exp[j(\omega_d t - \phi)] = R I \exp[j(\omega_d t - \phi)].$$

- Rearranging gives:

$$\mathcal{E}_m \exp[j\omega_d t] = I \exp[j(\omega_d t - \phi)] \times \left(R + j\omega_d L + \frac{1}{j\omega_d C} \right).$$

- Using $j^2 = -1$:

$$\mathcal{E}_m \exp[j\omega_d t] = I \exp[j(\omega_d t - \phi)] \times \left(R + j \left(\omega_d L - \frac{1}{\omega_d C} \right) \right).$$

Complex Numbers and AC Circuits

- We see the equation

$$\mathcal{E}_m \exp[j\omega_d t] = I \exp[j(\omega_d t - \phi)] \times \left(R + j \left(\omega_d L - \frac{1}{\omega_d C} \right) \right),$$

has the form $\mathcal{E} = \mathbf{i} \mathbf{Z}$, where \mathbf{Z} is the quantity:

$$\mathbf{Z} = R + j \left(\omega_d L - \frac{1}{\omega_d C} \right).$$


- \mathbf{Z} , the complex impedance, can be expressed in the alternative form:

$$\mathbf{Z} = Z \exp[j\phi], \text{ where:}$$

$$Z = \sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2} \text{ and}$$

$$\phi = \tan^{-1} \left(\frac{\omega_d L - 1/\omega_d C}{R} \right).$$

- In the Argand diagram:

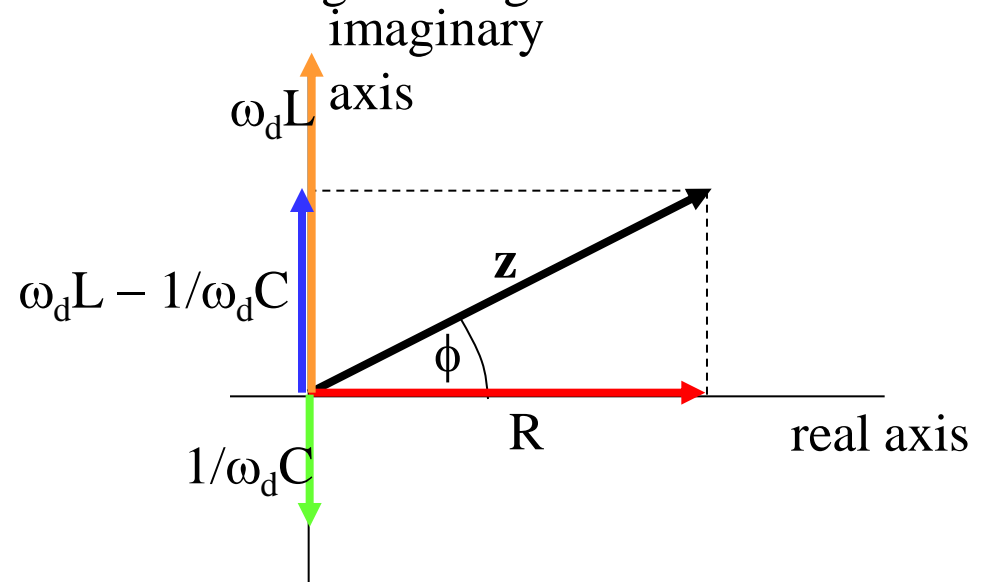

- See similarity to phasor approach.
- Resistive component of \mathbf{Z} same phase as \mathcal{E} , inductive component leads and capacitive component lags \mathcal{E} by $\pi/2$.
- Voltages associated with these components behave similarly.

Complex Impedance and Circuits with only R or L

- For resistor:

$$\mathbf{Z} = R + j0 \Rightarrow Z = \sqrt{R^2 + 0^2} = R$$

and $\phi = \tan^{-1}(0/R) = 0$.

- From $\mathcal{E} = \mathbf{i} \mathbf{Z}$ can calculate complex current:

$$\mathbf{i} = \frac{\mathcal{E}}{\mathbf{Z}} = \frac{\mathcal{E}_m \exp[j\omega_d t]}{Z \exp[j0]} = \frac{\mathcal{E}_m}{R} \exp[j\omega_d t].$$

- The current through the circuit is given by the real part of this:

$$i = \text{Re}(\mathbf{i}) = \frac{\mathcal{E}_m}{R} \cos(\omega_d t).$$

- This is in phase with the emf, remember here $\mathcal{E} = \mathcal{E}_m \cos(\omega_d t)$, and has amplitude \mathcal{E}_m/R as we expect.

- For inductor:

$$\mathbf{Z} = 0 + j\omega_d L \Rightarrow Z = \sqrt{0^2 + (\omega_d L)^2} = \omega_d L$$

and $\phi = \tan^{-1}(\omega_d L/0) = \pi/2$.

- Current:

$$\mathbf{i} = \frac{\mathcal{E}}{\mathbf{Z}} = \frac{\mathcal{E}_m \exp[j\omega_d t]}{Z \exp[j\pi/2]} = \frac{\mathcal{E}_m}{\omega_d L} \exp[j(\omega_d t - \pi/2)].$$

- Take real part of this:

$$i = \text{Re}(\mathbf{i}) = \frac{\mathcal{E}_m}{\omega_d L} \cos(\omega_d t - \pi/2).$$

- Again, result is as expected: current lags behind emf by $\pi/2$ and has amplitude $\mathcal{E}_m/\omega_d L$.

Complex Impedance with only C: General Circuits

- For capacitor:

$$\mathbf{Z} = 0 - j/\omega_d L$$

$$\Rightarrow Z = \sqrt{0^2 + (1/\omega_d C)^2} = 1/(\omega_d C)^2$$

$$\text{and } \phi = \tan^{-1}\left(\frac{-1/\omega_d C}{0}\right) = -\frac{\pi}{2}.$$

- Current: $\mathbf{i} = \frac{\mathcal{E}}{\mathbf{Z}} = \frac{\mathcal{E}_m \exp[j\omega_d t]}{Z \exp[-j\pi/2]}$
$$= \frac{\mathcal{E}_m}{1/\omega_d C} \exp[j(\omega_d t + \pi/2)].$$

- Take real part of this:

$$i = \text{Re}(\mathbf{i}) = \frac{\mathcal{E}_m}{1/\omega_d C} \cos(\omega_d t + \pi/2).$$

- As expected: current leads emf by $\pi/2$ and has amplitude $\mathcal{E}_m/(1/\omega_d C)$.

- For general AC circuit:

- Determine impedance of each component.

- Combine to give total impedance:

- ◆ Series $\mathbf{Z}_{\text{total}} = \sum_i \mathbf{Z}_i$.

- ◆ Parallel $\frac{1}{\mathbf{Z}_{\text{total}}} = \sum_i \frac{1}{\mathbf{Z}_i}$.

- Complex current from $\mathbf{i} = \mathcal{E}/\mathbf{Z}_{\text{total}}$.

- Amplitudes and phases from:

$$\frac{\mathcal{E}_m}{I} = |\mathbf{Z}_{\text{total}}| \text{ and } \tan^{-1}\left(\frac{\text{Im}(\mathbf{Z}_{\text{total}})}{\text{Re}(\mathbf{Z}_{\text{total}})}\right).$$

- Current from $\text{Re}(\mathbf{i})$.


Complex Impedance and Series LCR Circuit

■ Complex impedances:

◆ $\mathbf{Z}_R = R.$

◆ $\mathbf{Z}_L = j\omega_d L.$

◆ $\mathbf{Z}_C = -j/\omega_d C.$

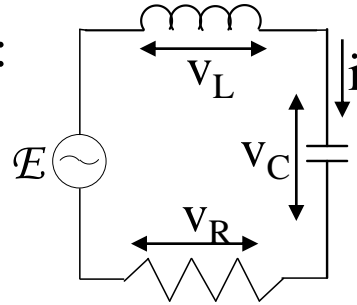

■ Add in series: $\mathbf{Z}_{\text{total}} = \mathbf{Z}_R + \mathbf{Z}_L + \mathbf{Z}_C$
 $= R + j\omega_d L - j/\omega_d C$
 $= R + j(\omega_d L - 1/\omega_d C).$

■ Hence:

◆ $Z_{\text{total}} = |\mathbf{Z}_{\text{total}}| = \sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}.$

◆ $\phi = \tan^{-1} \left(\frac{\text{Im}(\mathbf{Z}_{\text{total}})}{\text{Re}(\mathbf{Z}_{\text{total}})} \right)$
 $= \tan^{-1} \left(\frac{\omega_d L - 1/\omega_d C}{R} \right).$

■ Current:

$$i = \text{Re}(\mathbf{i}) = \text{Re} \left(\frac{\mathcal{E}}{\mathbf{Z}_{\text{total}}} \right)$$

$$= \text{Re} \left(\frac{\mathcal{E}_m \exp[j\omega_d t]}{\mathbf{Z}_{\text{total}} \exp[j\phi]} \right)$$

$$= \text{Re} \left(\frac{\mathcal{E}_m}{\mathbf{Z}_{\text{total}}} \exp[j(\omega_d t - \phi)] \right)$$

$$= \frac{\mathcal{E}_m}{Z_{\text{total}}} \cos(\omega_d t - \phi).$$