

Department of Physics
Year 1 Tutorials
Module Phys123
Electricity and Magnetism
Tutorial 5




Issued
Hand in to tutors
Tutorials

Thursday 2nd December
Wednesday 8th December 16:00
Friday 10th December

See the Year 1 Notice Board for tutorial groups, tutors, locations and times of tutorials.

Problems

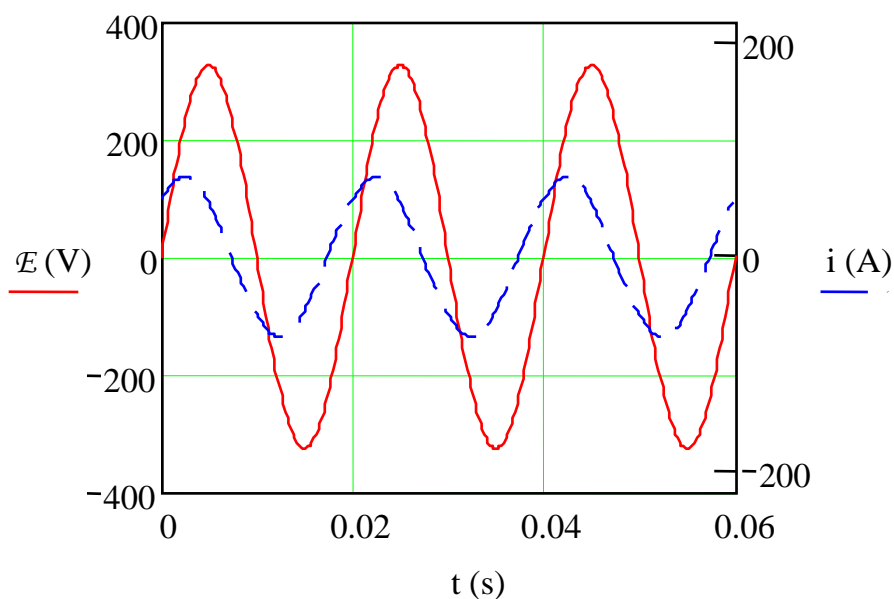1. An alternating current with an amplitude of 5 A is flowing through a $10\ \Omega$ resistor. What power is dissipated in the resistor?
2. An alternating voltage with an amplitude of 30 V and a frequency of 1 kHz is applied in turn across: a) a $50\ \Omega$ resistor; b) a 250 mH inductor; and c) a $1.5\ \mu\text{F}$ capacitor. What is the amplitude of the resulting current in each case? What is the power dissipated in each case?
3. The figure below shows the applied voltage \mathcal{E} (solid line) and the current i (dashed line) for a series LCR circuit.
 - a. Does the current lead or lag the applied voltage?
 - b. Is the circuit acting mainly inductively or mainly capacitively?
 - c. Is the frequency of the applied voltage greater or less than the resonant frequency of the circuit?



4. A series circuit consists of a capacitor $C = 1 \text{ nF}$, an inductor $L = 10 \text{ } \mu\text{H}$, a resistor $R = 10 \text{ } \Omega$ and a variable frequency power supply having a voltage amplitude of 10 V and zero internal resistance. Initially, the angular frequency is set to $\omega_d = 2 \times 10^6 \text{ rad sec}^{-1}$.
- Calculate values for the reactances of both the capacitor and the inductor.
 - Calculate the phase angle by which the current leads the voltage.
 - Calculate the magnitude of the impedance of the circuit.
 - The frequency of the power supply is now varied. Sketch a graph of the current amplitude I against the angular frequency ω_d . At what value of the angular frequency will the current amplitude be a maximum and what is the value of that maximum current amplitude?