


Lecture 10

- In this lecture we will look at:
 - ◆ Electromotive force.
 - ◆ Calculating the current in a circuit using the energy and potential methods.
 - ◆ Internal resistance.
 - ◆ Resistances in parallel.
 - ◆ Resistances in multi-loop circuits.
- After this lecture, you should be able to answer the following questions:
 - State Kirchoff's voltage and current rules: what alternative names are used for these rules?
 - What is the current in a circuit in which resistors of $3\ \Omega$ and $5\ \Omega$ are connected in parallel with an emf of $9\ \text{V}$ which has an internal resistance of $0.5\ \Omega$?
 - Describe how the loop and junction rules can be used to determine the current in a circuit consisting of a network of resistors and emfs.

Electromotive Force

- In order to make charge carriers flow round a circuit, an “electromotive force” or emf is needed.
- The job of a device providing an emf is to do work on the charges, pushing them through the resistance of the circuit.
- Common emf devices are:
 - ◆ Batteries.
 - ◆ Solar cells.
 - ◆ Generators.
- All of these convert energy (chemical, light, mechanical) into electrical energy.

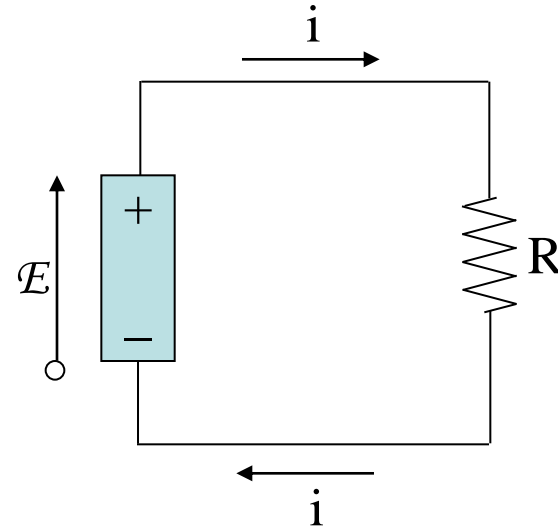
- Consider circuit with emf \mathcal{E} :



- Within the emf, +ive charges move from low potential to high potential against the electric field.
- The emf does an amount of work dW in moving a charge dq , define \mathcal{E} as:
$$\mathcal{E} = \frac{dW}{dq} \text{ (units } \text{J C}^{-1} = \text{V).}$$

Calculating the Current in a Circuit – Energy Method

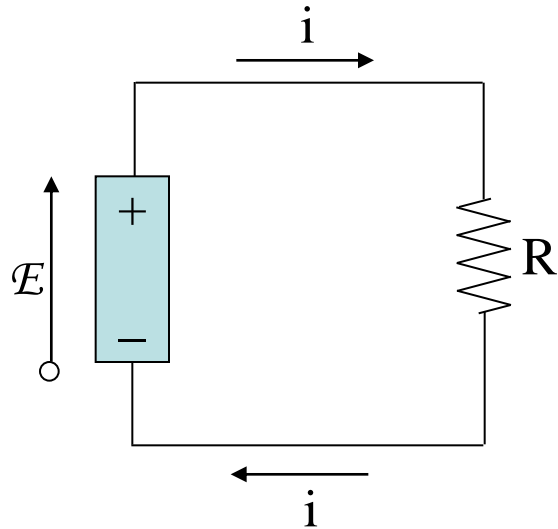- Consider a simple loop circuit containing an ideal emf and a resistor, connected with wires of negligible resistance:




- We know $P = i^2R$, so in an interval dt , an amount of energy $i^2R dt$ will appear in the resistor.

- During this time, a charge $dq = i dt$ will have moved through the emf.
- The emf will have done an amount of work $dW = \mathcal{E} dq = \mathcal{E} i dt$ on the charge.
- The work done by the emf must equal the energy appearing in the resistor.
- Hence $\mathcal{E} = iR$.
- Solving for the current:

$$i = \frac{\mathcal{E}}{R} \quad [10.1]$$

Current – Potential Method or Kirchoff's Voltage Rule

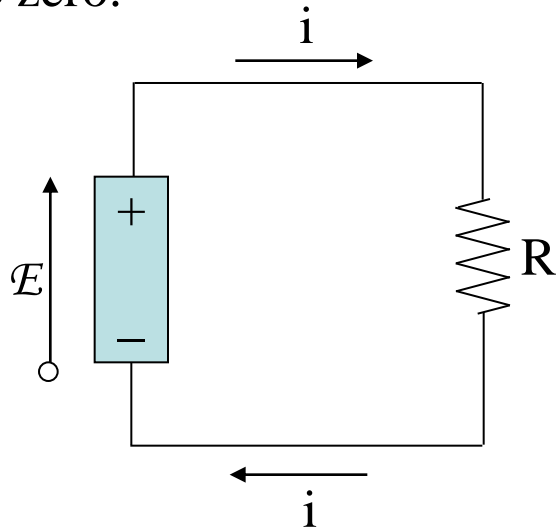- Start at any point in the circuit and work round it, adding all the potential differences you come across.
- Kirchoff's voltage rule (or loop rule): The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero.



- Start at –ive terminal of emf, which we assume has a potential V_- .
- Move to +ive terminal, potential difference is \mathcal{E} .
- Move along wires, no potential change as these have negligible resistance.
- Move through the resistor, potential difference is $-iR$.
- Move along wires, no potential change as these have negligible resistance.
- Arrive back at point with potential V_- .
- From Kirchoff's law:

$$V_- + \mathcal{E} - iR = V_- \Rightarrow \mathcal{E} - iR = 0$$

$$\Rightarrow i = \frac{\mathcal{E}}{R}$$

Internal Resistance


- For our ideal emf: $\mathcal{E} = iR$.
- Any real emf device has an internal resistance r , so

$$\mathcal{E} = iR + ir \quad [10.2]$$

potential
across
external R


potential
across
internal r

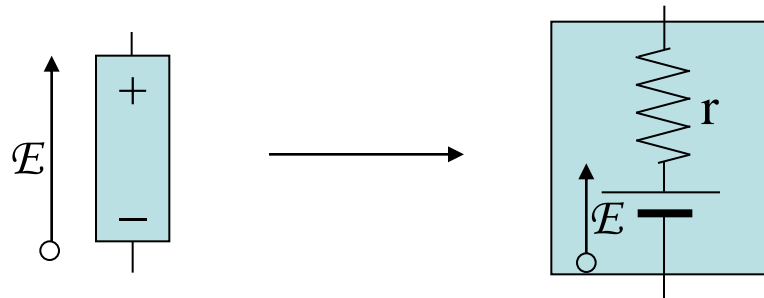- An ideal emf will always have a potential across its terminals equal to its nominal value (e.g. 12 V for an ideal 12 V battery).
- A real emf will only have its nominal potential across its terminals when no current is flowing.



Resistance in More Complex Circuits

- Add internal resistance:

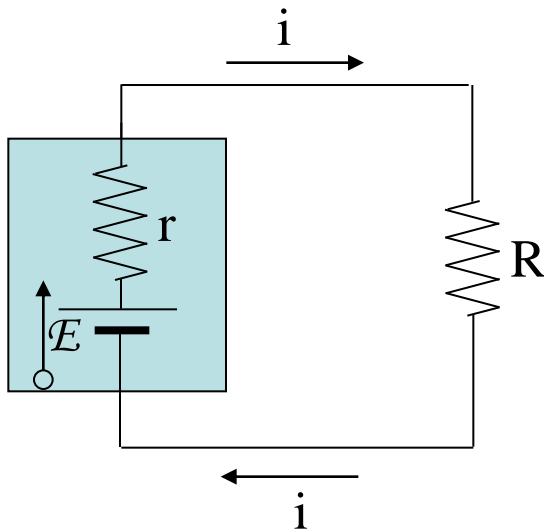

- Now get:

$$V_- + \mathcal{E} - ir - iR = V_-$$

$$\Rightarrow \mathcal{E} - i(r + R) = 0$$

$$\Rightarrow i = \frac{\mathcal{E}}{r + R} \quad [10.3]$$

- Add other resistances:

- An identical current i flows through each resistance.



- Hence

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$

$$\Rightarrow i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}.$$

- The combination of resistors can be replaced by an equivalent resistance


$$R_{\text{eq}} = R_1 + R_2 + R_3$$

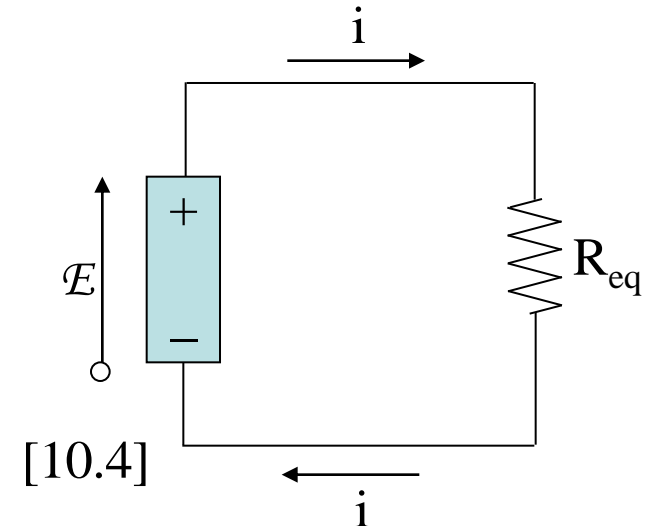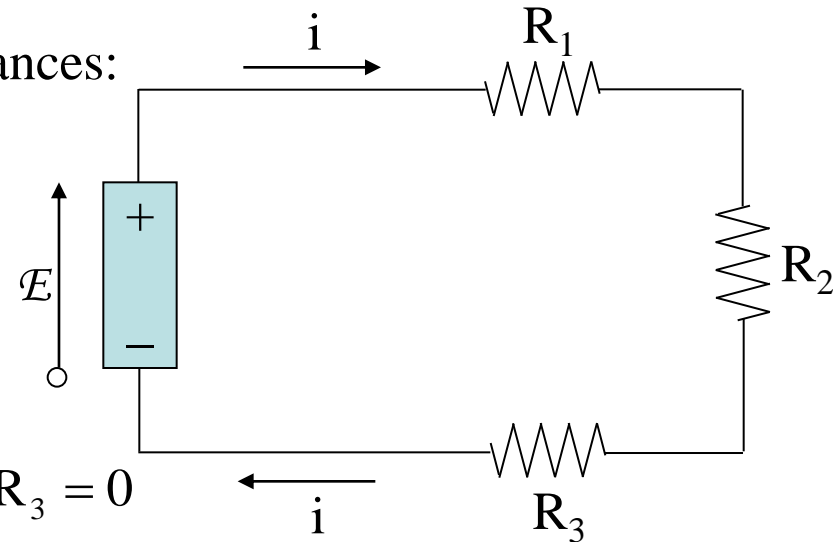

[10.4]

Resistors in Parallel – Kirchoff's Current Rule

- Consider the following circuit:

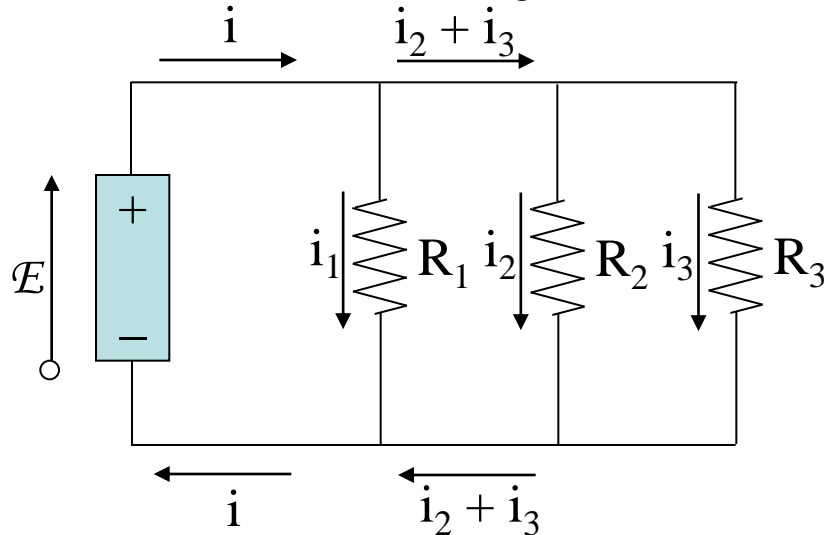

- We can see Kirchoff's current rule (or junction rule) must apply: The sum of the currents entering any junction must be equal to the sum of the currents leaving the junction.

- This tells us: $i = i_1 + i_2 + i_3$.

- We also know that:

$$i_1 = \mathcal{E}/R_1, \quad i_2 = \mathcal{E}/R_2 \quad \text{and} \quad i_3 = \mathcal{E}/R_3.$$


- Substituting these in the above:

$$i = i_1 + i_2 + i_3 = \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2} + \frac{\mathcal{E}}{R_3}.$$

- The equivalent resistance for parallel resistors can then be found from:


$$\frac{\mathcal{E}}{R_{\text{eq}}} = \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2} + \frac{\mathcal{E}}{R_3}, \text{ i.e.}$$
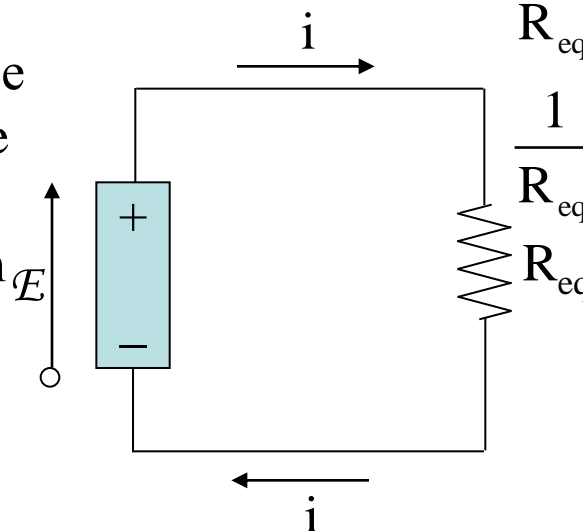
$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad [10.5]$$



Multi-loop Circuits

- Consider the circuit:

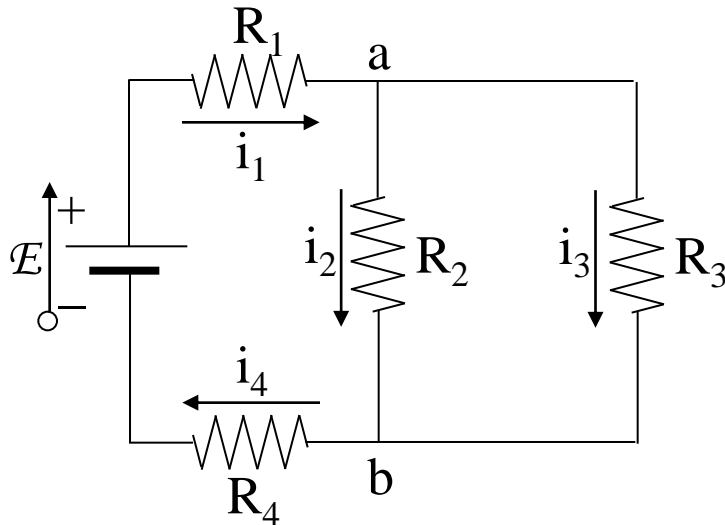

- Use loop rule LH loop:

$$\mathcal{E} = i_1 R_1 + i_2 R_2 + i_4 R_4 \quad (1).$$

- Now for RH loop:

$$i_2 R_2 = i_3 R_3 \quad (2).$$

- For outermost loop:

$$\mathcal{E} = i_1 R_1 + i_3 R_3 + i_4 R_4 \quad (3).$$

- Now use junction rule at point a:

$$i_1 = i_2 + i_3 \quad (4).$$

- And at point b:

$$i_4 = i_2 + i_3 \quad (5).$$

- Now have 5 equations for 4 unknowns, solve for i_1 , i_2 , i_3 and i_4 .

- From (2) $i_2 = i_3 R_3 / R_2$ or $i_3 = i_2 R_2 / R_3$.

- From (4) $i_1 = i_3 \frac{R_3}{R_2} + i_3 = i_3 \left(\frac{R_2 + R_3}{R_2} \right)$.

- From (4) and (5) $i_4 = i_1$, but also $i_4 = i_3 (R_3 / R_2 + 1)$.

- From (1) and above:

$$\mathcal{E} = i_1 R_1 + i_3 R_2 \frac{R_3}{R_2} + i_1 R_4.$$

Multi-loop Circuits

- Substituting for i_3 and rearranging:

$$\begin{aligned}\mathcal{E} &= i_1 R_1 + i_1 \frac{R_2}{R_2 + R_3} \frac{R_2 R_3}{R_2} + i_1 R_4 \\ &= i_1 R_1 + i_1 \frac{R_2}{R_2 + R_3} R_3 + i_1 R_4 \\ &= i_1 \left(\frac{R_1(R_2 + R_3) + R_2 R_3 + R_4(R_2 + R_3)}{R_2 + R_3} \right) \\ \Rightarrow i_1 &= \frac{\mathcal{E} (R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3 + R_2 R_4 + R_3 R_4}.\end{aligned}$$

- Strategy: use junction rule at every junction to give minimum number of unknown currents.
- Apply loop rule around same number of different loops as there are unknown currents.
- Solve equations for currents.

- For some circuits there may be better (simpler) strategies...

- E.g. here can find equivalent resistance due to R_2 and R_3 as these are in parallel:

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{R_2 + R_3}{R_2 R_3}.$$

- Total equivalent resistance is then

$$\begin{aligned}R_{\text{eq}} &= R_1 + R_{23} + R_4 \\ &= R_1 + \frac{R_2 R_3}{R_2 + R_3} + R_4 \\ &= \frac{R_1(R_2 + R_3) + R_2 R_3 + R_4(R_2 + R_3)}{R_2 + R_3}\end{aligned}$$

- Hence total current is

$$i_1 = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{\mathcal{E}(R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3 + R_2 R_4 + R_3 R_4}.$$