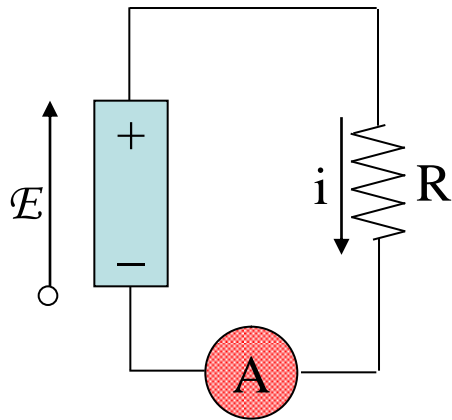


Lecture 11


- In this lecture we will look at:
 - ◆ Measuring currents
 - ◆ Measuring potentials.
 - ◆ Circuits with resistance and capacitance.
- After this lecture, you should be able to answer the following questions:
 - Explain why the resistance of an ammeter must be small and the resistance of a voltmeter large.
 - Write down the equation describing how the current in a series circuit containing a capacitance C , a resistance R , an emf \mathcal{E} and a switch changes from the instant that the switch is closed.

Measuring Current

- The ammeter is used to measure current.
- Must be inserted in the circuit (in series) at the point at which the current is to be measured.



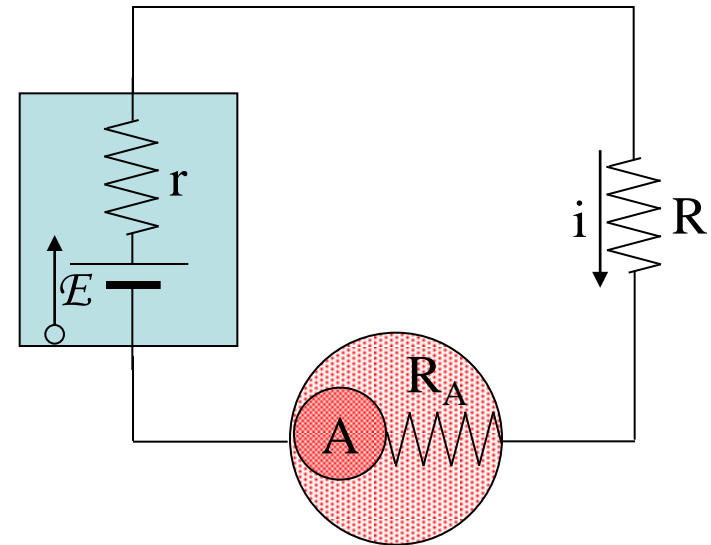
- The resistance of the ammeter, R_A , must be small ($R_A \ll R + r$) otherwise the meter causes a change in the current.



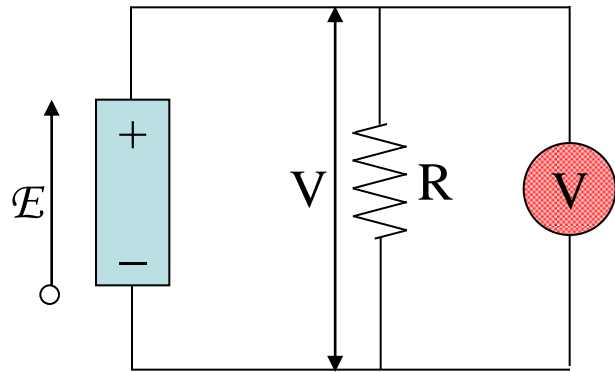
- Example, if $R = 1 \text{ k}\Omega$, $r = 200 \text{ }\Omega$, $R_A = 10 \text{ }\Omega$ and $\mathcal{E} = 12 \text{ V}$:
 - ◆ $i = 12/1200 = 10 \text{ mA}$ before insertion of ammeter...
 - ◆ ...and afterwards
$$i' = \frac{12}{1000 + 200 + 10} = 9.92 \text{ mA.}$$

Measuring Potential

- The voltmeter is used to measure potential.
- Must be connected across (in parallel with) the component over which the potential is to be measured.



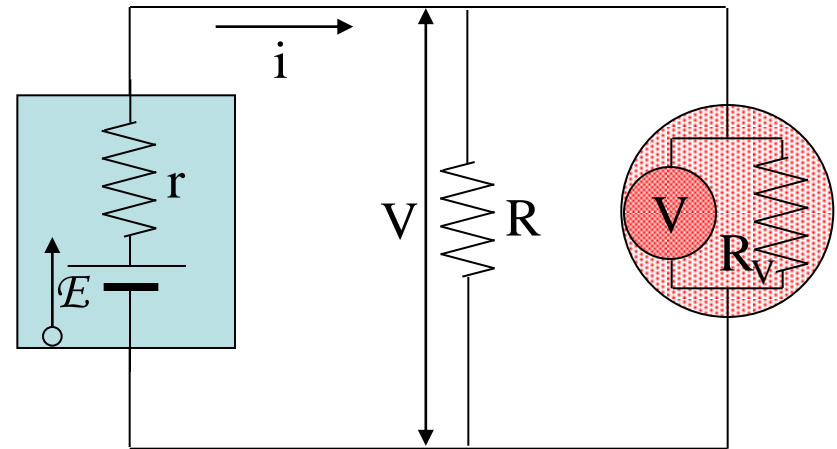- The resistance of the voltmeter, R_V , must be large ($R_V \gg R + r$) otherwise the meter changes V .



- Example, if $R = 1 \text{ k}\Omega$, $r = 200 \text{ }\Omega$, $R_V = 100 \text{ k}\Omega$ and $\mathcal{E} = 12 \text{ V}$:
- Before insertion of voltmeter $i = 10 \text{ mA}$, so $V = 0.01 \times 1000 = 10 \text{ V}$.
- Afterwards the resistance seen by \mathcal{E} is:

$$R_{\text{eq}} = r + \left(\frac{1}{R} + \frac{1}{R_V} \right)^{-1} = r + \frac{R R_V}{R + R_V}$$

$$= \frac{r(R + R_V) + R R_V}{R + R_V} = 1190.1 \Omega.$$


Measuring Potential

- Hence new current:

$$i' = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{12}{1190} = 10.08 \text{ mA.}$$

- The resistance over which the potential is measured is:
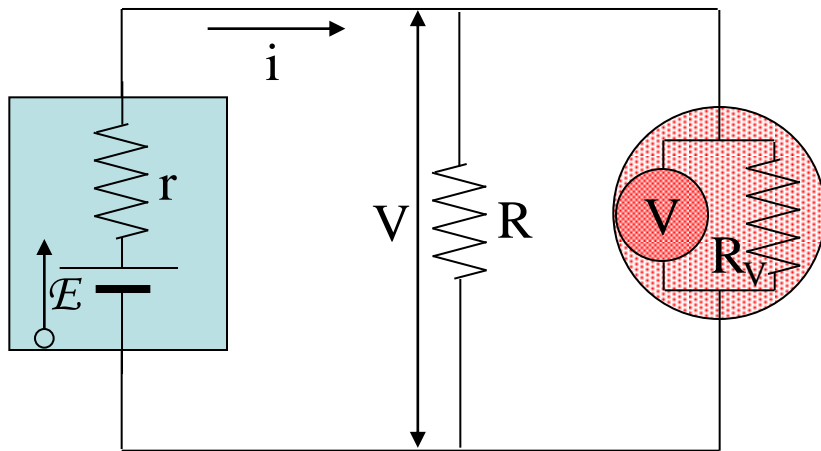
$$R' = \left(\frac{1}{R} + \frac{1}{R_v} \right)^{-1} = \frac{R R_v}{R + R_v} = 990.1 \Omega.$$



- From these we obtain potential measured by voltmeter:

$$V' = i' R'$$

$$\begin{aligned} &= \frac{\mathcal{E}}{r(R + R_v) + R R_v} \frac{R R_v}{R + R_v} \\ &= \frac{\mathcal{E} R R_v}{r(R + R_v) + R R_v}. \end{aligned}$$

- Numerically,


$$\begin{aligned} V' &= i' R' \\ &= 0.01008 \times 990 \\ &= 9.98 \text{ V.} \end{aligned}$$

- Note “potential divider”:

$$V_{R'} = 12 \times 990.1 / 1190, \quad V_r = 12 \times 200 / 1190.$$

Circuits with Resistance and Capacitance

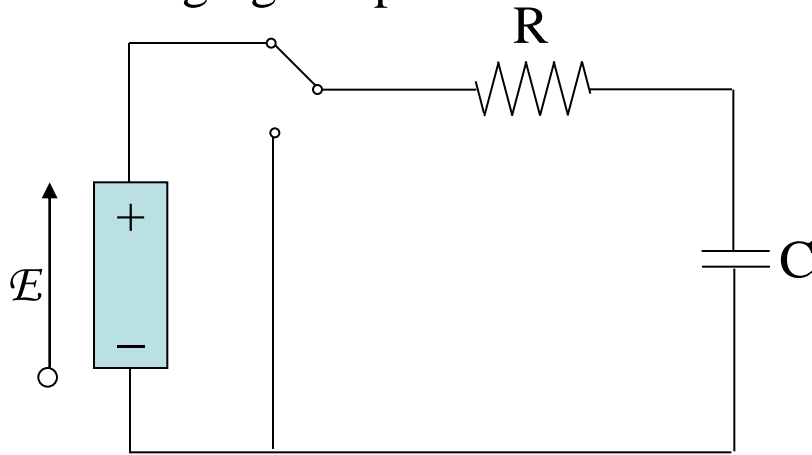- First consideration of circuits in which current varies with time: charging a capacitor.



- Potential across capacitor
 $V_C(t) = q(t)/C.$
- Potential across resistor
 $V_R(t) = i(t) R.$
- Note these change with time!

- Applying Kirchoff's loop rule:

$$\mathcal{E} - i(t)R - \frac{q(t)}{C} = 0.$$

- Cannot solve as contains two variables, $i(t)$ and $q(t)$.

- However: $i = \frac{dq}{dt}.$

- Hence, $R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}$ [11.1]

- Try solution:
 $q = C\mathcal{E}(1 - \exp(-t/RC)).$

- Differentiating:

$$\frac{dq}{dt} = \frac{\mathcal{E}}{R} \exp(-t/RC)$$

Circuits with Resistance and Capacitance

- Substitute into equation to check have solution.

- $$R \frac{dq}{dt} + \frac{q}{C}$$
$$= R \frac{\mathcal{E}}{R} \exp\left[-\frac{t}{RC}\right] + \frac{1}{C} C \mathcal{E} \left(1 - \exp\left[-\frac{t}{RC}\right]\right)$$
$$= \mathcal{E} \exp\left[-\frac{t}{RC}\right] + \mathcal{E} - \mathcal{E} \exp\left[-\frac{t}{RC}\right]$$
$$= \mathcal{E}, \text{ QED.}$$

- The quantity $\tau = RC$ is the time constant of the circuit: units seconds.
- Using $q = CV$ see solution can be written:

$$V_C = \frac{q}{C} = \mathcal{E} (1 - \exp(-t / RC)) \quad [11.2]$$

- The differential w.r.t. time is the current through the circuit:


$$i(t) = \frac{dq}{dt} = \frac{\mathcal{E}}{R} \exp(-t / RC) \quad [11.3]$$

- Check get expected limits:

- ◆ $q(0) = 0.$
- ◆ $V(0) = 0.$
- ◆ $i(0) = \mathcal{E}/R$, (i.e. maximum current when switch first closed).
- ◆ $q(\infty) = C\mathcal{E}.$
- ◆ $V(\infty) = \mathcal{E}.$
- ◆ $I(\infty) = 0.$

Circuits with Resistance and Capacitance

- Now think about discharging capacitor:

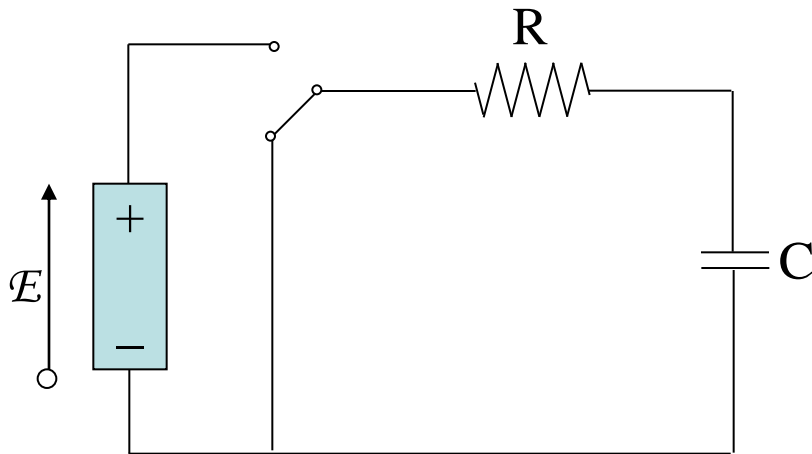

- Using Kirchoff's loop rule:

$$i(t)R + \frac{q(t)}{C} = 0 \text{ or}$$

$$R \frac{dq}{dt} + \frac{q}{C} = 0 \quad [11.4]$$

- Try solution $q = q_0 \exp(-t/RC)$.
- Differentiating and substituting we get:

$$\begin{aligned} R \frac{dq}{dt} + \frac{q}{C} \\ = -R \frac{q_0}{RC} \exp\left[-\frac{t}{RC}\right] + \frac{1}{C} q_0 \exp\left[-\frac{t}{RC}\right] \\ = 0, \text{ QED.} \end{aligned}$$


- Voltage across C, current in circuit:

$$\begin{aligned} V &= \frac{q}{C} = \frac{q_0}{C} \exp(-t/RC) \\ &= V_0 \exp(-t/RC) \quad [11.5] \end{aligned}$$

$$\begin{aligned} i &= \frac{dq}{dt} = -\frac{q_0}{RC} \exp(-t/RC) \\ &= i_0 \exp(-t/RC) \quad [11.6] \end{aligned}$$

Circuits with Resistance and Capacitance

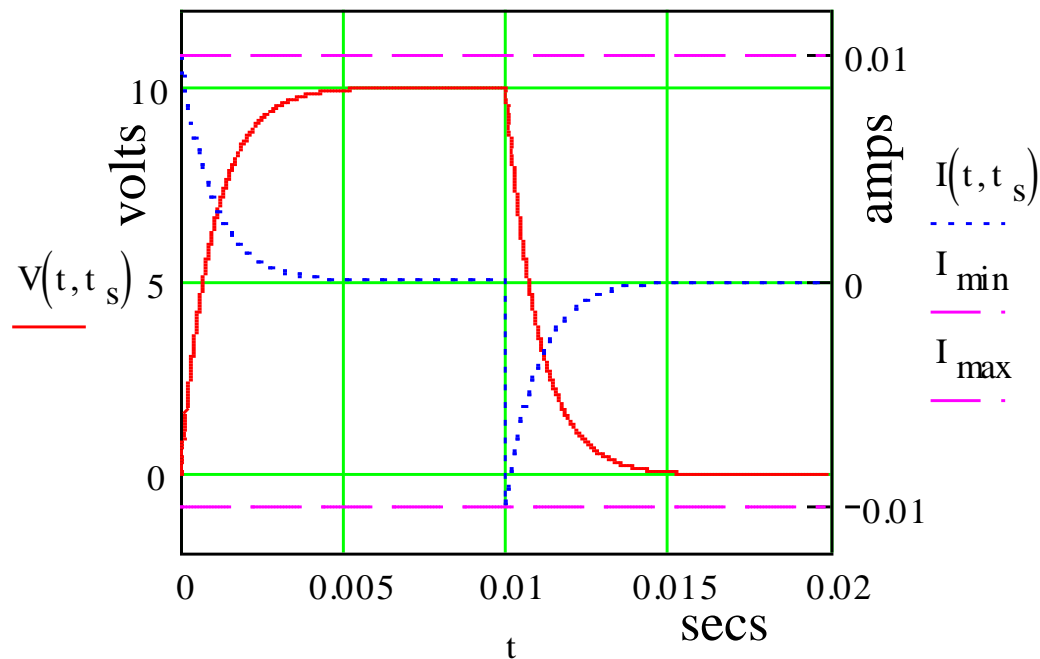- Look at example:
 - ◆ $R = 1 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$ so $\tau = 1 \text{ ms}$.
 - ◆ $\mathcal{E} = 10 \text{ V}$.
 - ◆ Charge for 10 ms, then discharge:



- If flip switch before charge “complete” (here at $t = 2\tau$):

