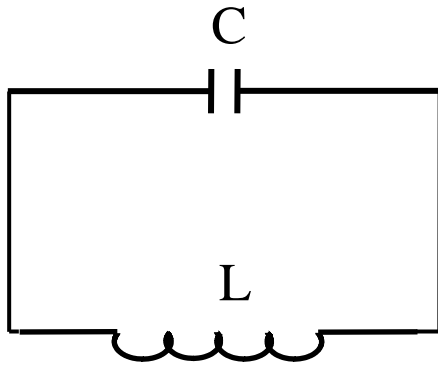


Lecture 18

- In this lecture we will look at:
 - ◆ Circuits containing capacitance and inductance.
 - ◆ Charge current and energy oscillations.
 - ◆ LCR circuits.
 - ◆ Damped charge, current and energy oscillations.
- After this lecture, you should be able to answer the following questions:
 - Write down the differential equation describing the charge oscillations of a circuit containing an inductance and a capacitance.
 - How does this equation change if a series resistance is introduced to the circuit?
 - Explain the behaviour of a lightly damped series LCR circuit, starting from the point at which the capacitor is charged and there is no current flowing in the circuit.

Electromagnetic Oscillations

- Look at circuits containing both capacitance and inductance.



- Have shown that energy stored in a capacitor and inductor given by:


- ◆ $U_E = \frac{q^2}{2C}$.

- ◆ $U_B = \frac{Li^2}{2}$.


- If start with capacitor charged, have energy in E field, energy density:
 $u_E = \frac{1}{2} \epsilon_0 E^2$.
- Capacitor will discharge through inductor.
- Current will cause build up of magnetic field, energy then stored in B field, energy density:
 $u_B = \frac{B^2}{2\mu_0}$.
- B field will then decay, inducing current and charging up capacitor...
- Note, using small letters for varying quantities (e.g. charge q) and large letters for constants (e.g. amplitude of charge oscillations, Q).

Electromagnetic Oscillations


■ 1

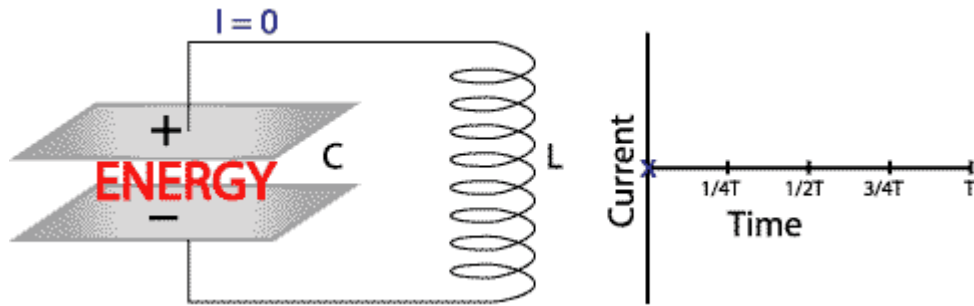


■ 3

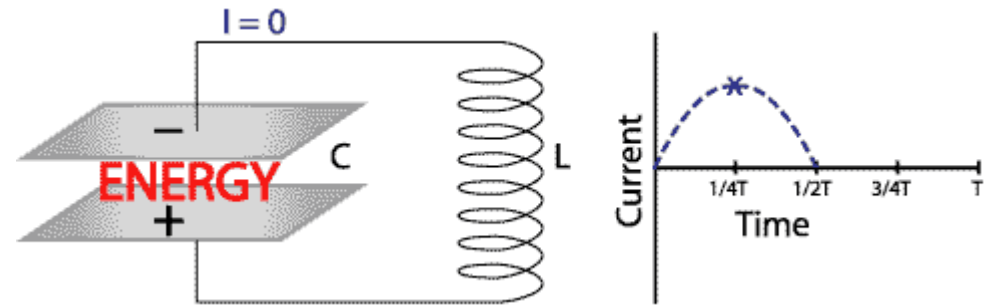

■ 2

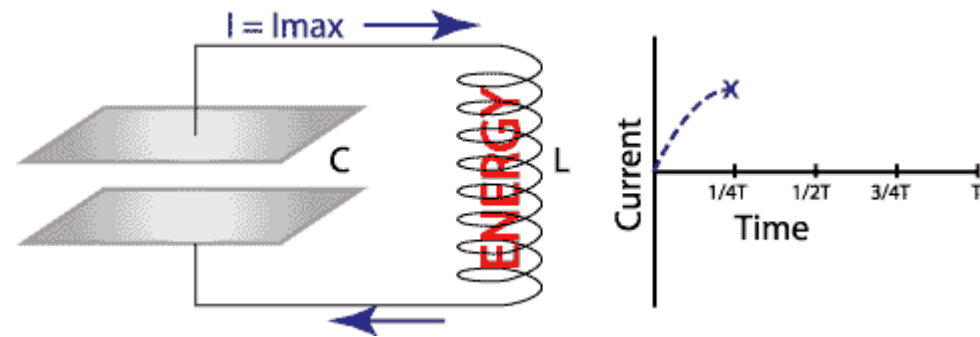

■ 4

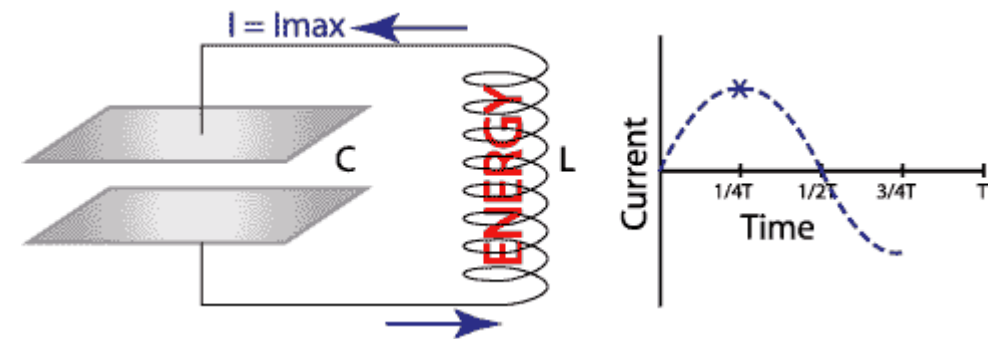

Energy in LC Circuit

- Total energy in L and C is:

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}.$$

- As no resistance in circuit, no energy is dissipated, that is:

$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{Li^2}{2} + \frac{q^2}{2C} \right) = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = 0.$$

- Making the substitutions:

$$i = \frac{dq}{dt} \text{ and } \frac{di}{dt} = \frac{d^2q}{dt^2},$$

we then have:

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0 \quad [18.1]$$

- This differential equation describes the oscillations of the LC circuit.

- Try solution $q = Q \cos(\omega t + \phi)$ [18.2]

- Calculate derivatives:

$$\frac{dq}{dt} = -Q\omega \sin(\omega t + \phi),$$

$$\frac{d^2q}{dt^2} = -Q\omega^2 \cos(\omega t + \phi).$$

- Substitute into differential equation:

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0$$

$$\Rightarrow -\omega^2 LQ \cos(\omega t + \phi) + \frac{Q}{C} \cos(\omega t + \phi) = 0$$

$$\text{or } \left(-\omega^2 L + \frac{1}{C} \right) Q \cos(\omega t + \phi) = 0$$

$$\Rightarrow \omega^2 = \frac{1}{LC} \quad [18.3]$$

Charge and Current Oscillations

- Hence $q = Q \cos(\omega t + \phi)$ is solution of $L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0$ provided $\omega = \frac{1}{\sqrt{LC}}$.

- Thus the charge stored on the capacitor exhibits sinusoidal oscillations with frequency


$$f = \frac{1}{2\pi\sqrt{LC}}.$$

- Current in circuit is given by

$$i = \frac{dq}{dt} = -Q\omega \sin(\omega t + \phi) \quad [18.4]$$

- Hence current also shows sinusoidal oscillations, with amplitude $Q\omega$.

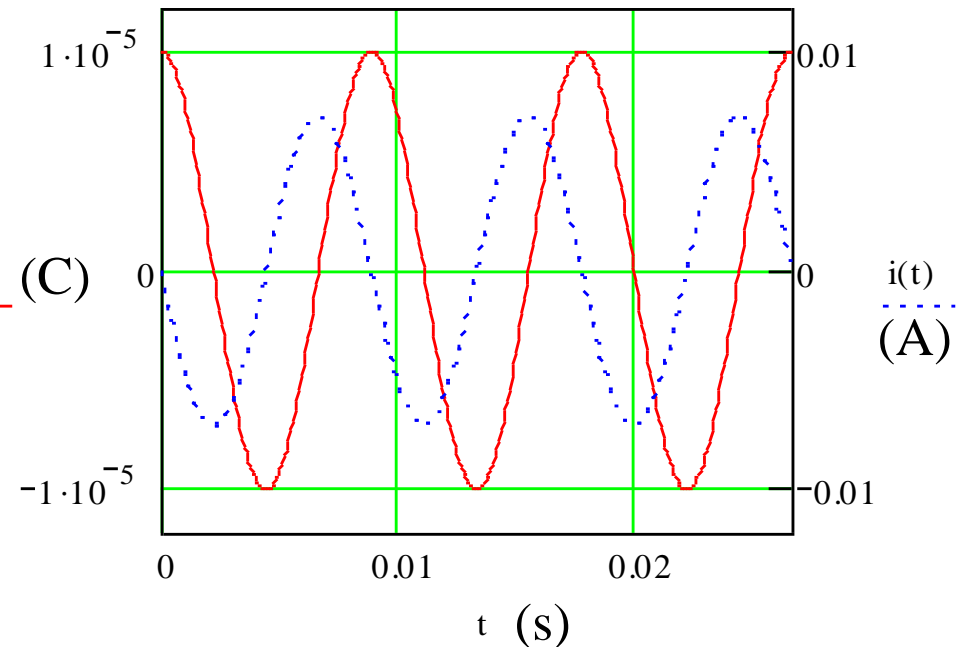- Graph of charge stored on capacitor and current in circuit, with $C = 10^{-6}$ F, $L = 2$ H (gives $f = 112$ Hz), charge on capacitor at $t = 0$ is 10^{-5} C (i.e. initial potential 10 V):



Energy Oscillations

- Can now check that total energy is conserved.
- Look at energy stored in E field in capacitor...

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$


- ...and at energy stored in B field in inductor:

$$U_B = \frac{Li^2}{2} = \frac{L\omega^2 Q^2 \sin^2(\omega t + \phi)}{2}$$

- Substituting for ω gives:

$$U_B = \frac{Li^2}{2} = \frac{Q^2}{2C} \sin^2(\omega t + \phi)$$

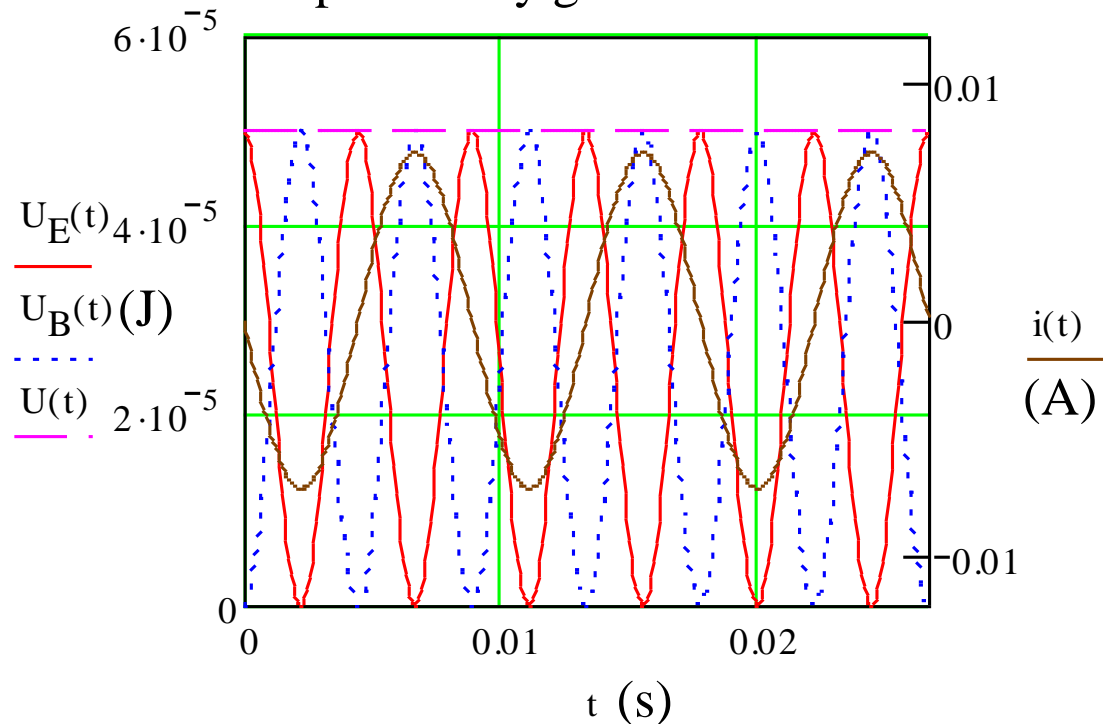
- Plotting these quantities and their sum, U , for the values of C , L and Q used previously gives:



- Notice total energy looks constant as expected: exercise, prove this!

RLC Circuit

- Now include resistance in the circuit:

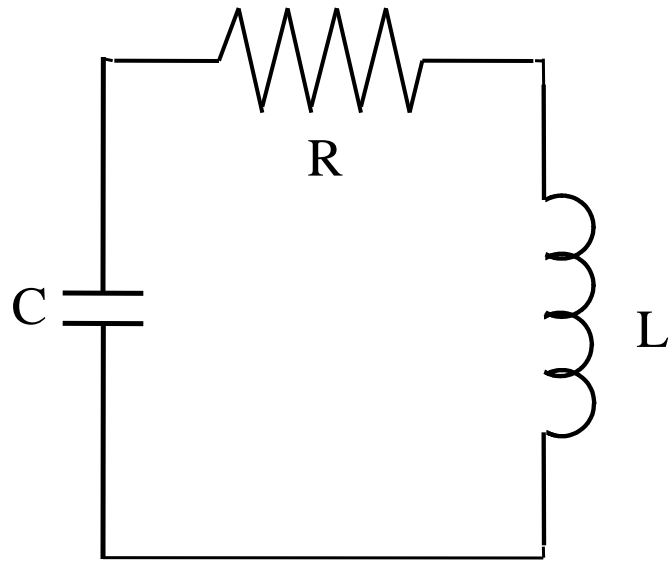

- The total electromagnetic energy, $U = U_E + U_B$, is now no longer constant as it is converted to heat in the resistor at a rate given by i^2R .

- That is:

$$\frac{dU}{dt} = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = -i^2R.$$

- Substituting for the current as before:

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C}q = 0 \quad [18.5]$$

- The solution to this equation is:

$$q = Q \exp\left[-\frac{Rt}{2L}\right] \cos(\omega't + \phi),$$

$$\text{where } \omega' = \sqrt{\omega^2 - (R/2L)^2} \quad [18.6]$$


- The amplitude of the charge oscillations decreases with time (i.e. they are damped) according to $Q \exp\left[-\frac{Rt}{2L}\right]$.

Damped Charge and Current Oscillations

- The (angular) frequency of the oscillations is also decreased.
- Consider situations in which $\omega \approx \omega'$, this is the case when the damping is not too strong.
- The current is given by:

$$\begin{aligned}\frac{dq}{dt} &= \frac{d}{dt} Q \exp\left[-\frac{Rt}{2L}\right] \cos(\omega't + \phi) \\ &= -\frac{R}{2L} Q \exp\left[-\frac{Rt}{2L}\right] \cos(\omega't + \phi) \\ &\quad - \omega' Q \exp\left[-\frac{Rt}{2L}\right] \sin(\omega't + \phi).\end{aligned}$$

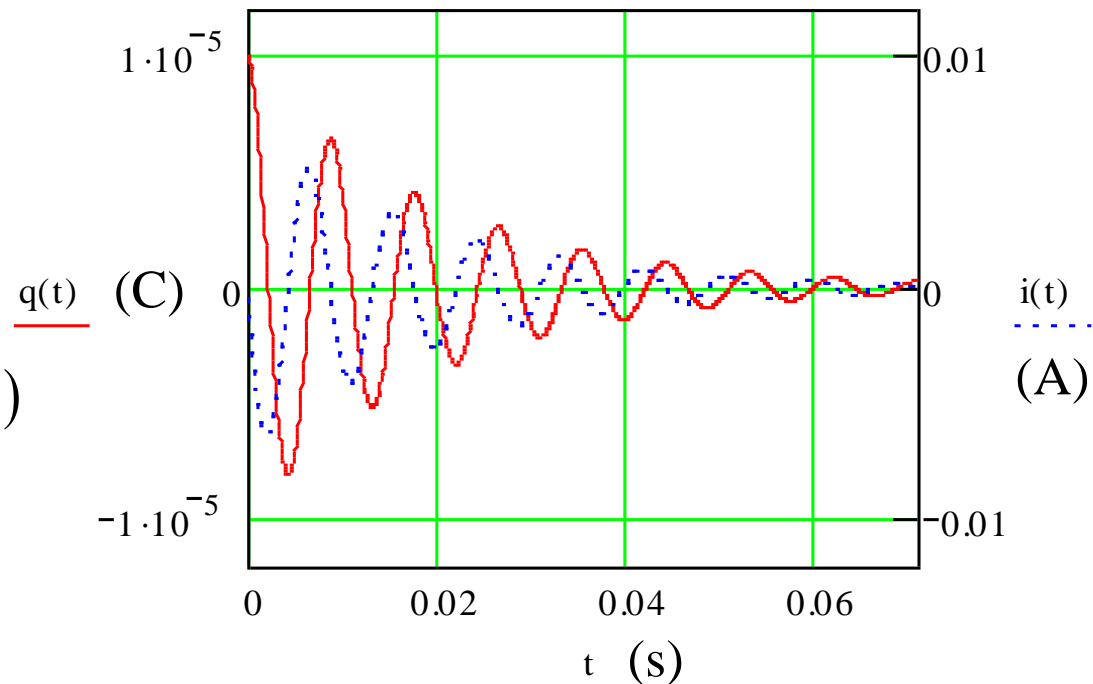
- With the same L and C values as before, adding a 200 Ω resistor, the current and charge behave as below:



Damped Energy Oscillations

- The energy stored in the electric field of the capacitor is given by:
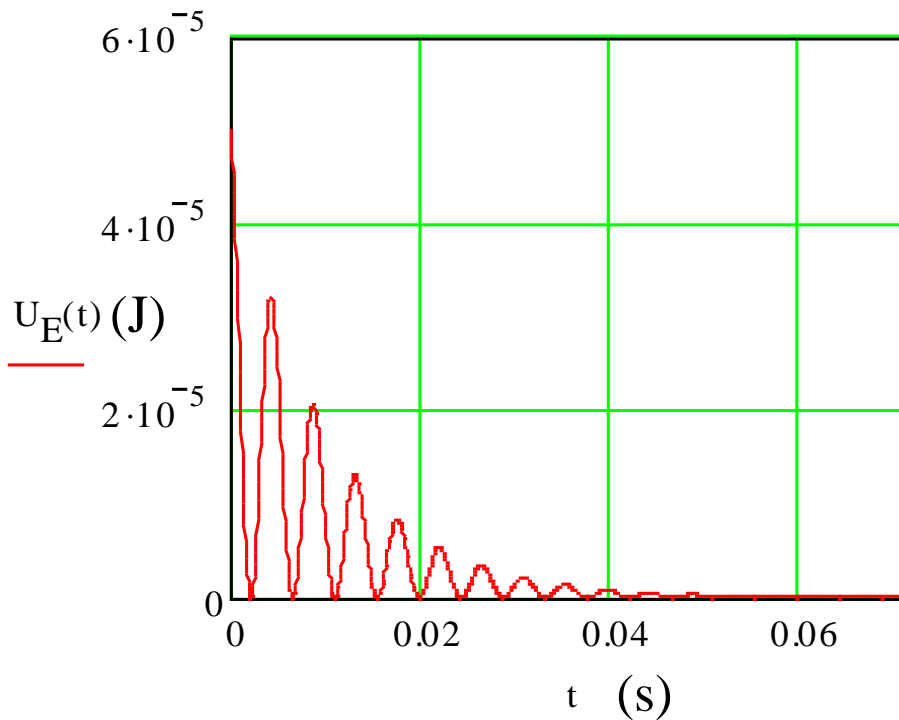
$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \exp\left[-\frac{Rt}{L}\right] \cos^2(\omega't + \phi).$$



- The expression for U_B is a little messy, but adding this and the total electromagnetic energy U to the plot gives:

