

Answers for Tutorial 5

The marks to be awarded for each question are indicated in square brackets.

Problem 1 [5]

$$I = 5 \text{ A, so } I_{\text{rms}} = 5/\sqrt{2} = 3.54 \text{ A.} \quad [2]$$

$$\text{Average power } P = I_{\text{rms}}^2 R = 5^2/2 \times 10 = 125 \text{ W.} \quad [3]$$

Problem 2 [10]

$$\mathcal{E} = 30 \text{ V.}$$

$$f = 1 \text{ kHz, so } \omega = 2\pi f = 6.28 \times 10^3 \text{ rad/sec}$$

$$\text{a) } I = \mathcal{E}/R = 30/50 = 0.6 \text{ A.} \quad [1]$$

$$P = I_{\text{rms}}^2 R = (0.6/\sqrt{2})^2 \times 50 = 9 \text{ W.} \quad [1]$$

$$\text{b) } \text{For inductor, } I = \mathcal{E}/\omega L = 30/(6.28 \times 10^3 \times 0.25) = 0.0191 \text{ A.} \quad [2]$$

$$\text{No power dissipated in inductor.} \quad [2]$$

$$\text{c) } \text{For capacitor, } I = \mathcal{E}/(1/\omega C) = 30 \times 6.28 \times 10^3 \times 1.5 \times 10^{-6} = 0.283 \text{ A.} \quad [2]$$

$$\text{No power dissipated in capacitor.} \quad [2]$$

Problem 3 [5]

$$\text{a) } \text{The current leads the voltage, i.e. the current peaks before the voltage.} \quad [1]$$

b) As the current leads the voltage, the phase ϕ in the expression $i = I \sin(\omega t - \phi)$ is negative. As this phase is given by $\phi = \tan^{-1}((\omega L - 1/\omega C)/R)$, the capacitive reactance $1/\omega C$ is larger than the inductive reactance ωL : the circuit is predominantly capacitive.

(Alternatively, i leads v , so from the mnemonic CiviL the circuit is capacitively dominated, the same conclusion is reached from the mnemonic $\mathcal{E}Li$ is positively the $iC\mathcal{E}$ man!) [2]

$$\text{c) } \text{The phase is negative below the resonant frequency and positive above, so from the above, the frequency is below the resonant frequency.} \quad [2]$$

Problem 4 [15]

$$\text{a) } X_C = 1/\omega_d C = 1/(2 \times 10^6 \times 1 \times 10^{-9}) = 500 \Omega. \quad [2]$$


$$X_L = \omega_d L = 2 \times 10^6 \times 10 \times 10^{-6} = 20 \Omega. \quad [2]$$

$$\text{b) } \phi = \tan^{-1}\left(\frac{\omega_d L - 1/\omega_d C}{R}\right) = \tan^{-1}\left(\frac{20 - 500}{10}\right) = -88.8^\circ \text{ or } -1.55 \text{ rad.} \quad [2]$$

Phase is negative, so current leads voltage by 88.8°

$$\text{c) } Z = \sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2} = 480 \Omega \text{ (contribution of resistance negligible).} \quad [2]$$

d) Sketch of shape of resonance.

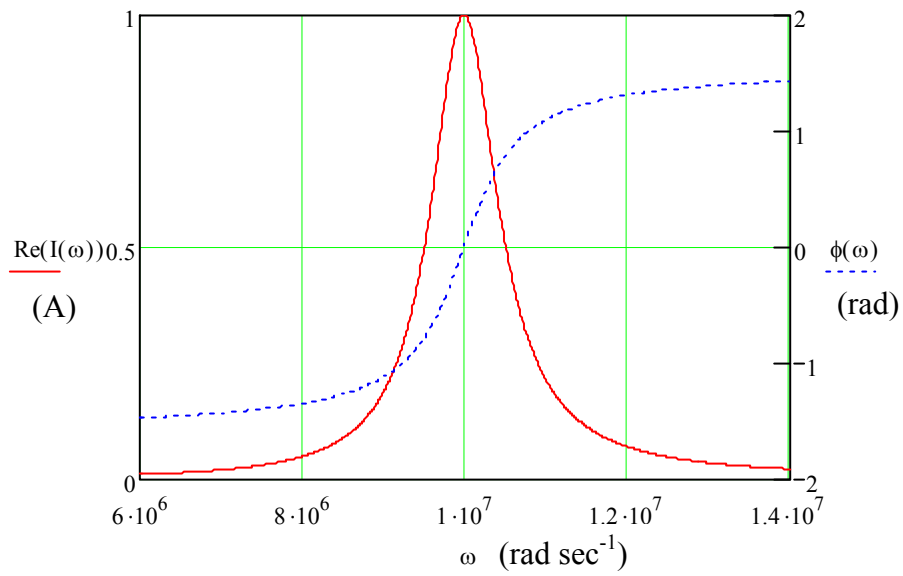

[3]

The current i has a maximum value of $I = \mathcal{E}/R = 10/10 = 1$ A,

[2]

at the resonant frequency $\omega = 1/\sqrt{LC} = 1/\sqrt{1 \times 10^{-9} \times 10 \times 10^{-6}} = 10^7$ rad sec⁻¹.

[2]

Maximum possible number of marks for this tutorial is 35.