
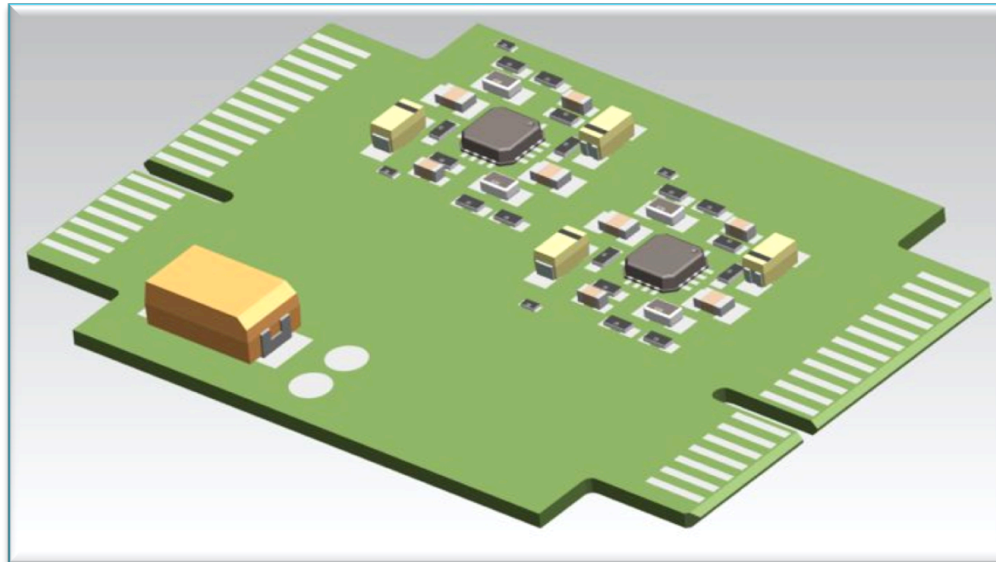


CHEC Detector Pre-amplifiers

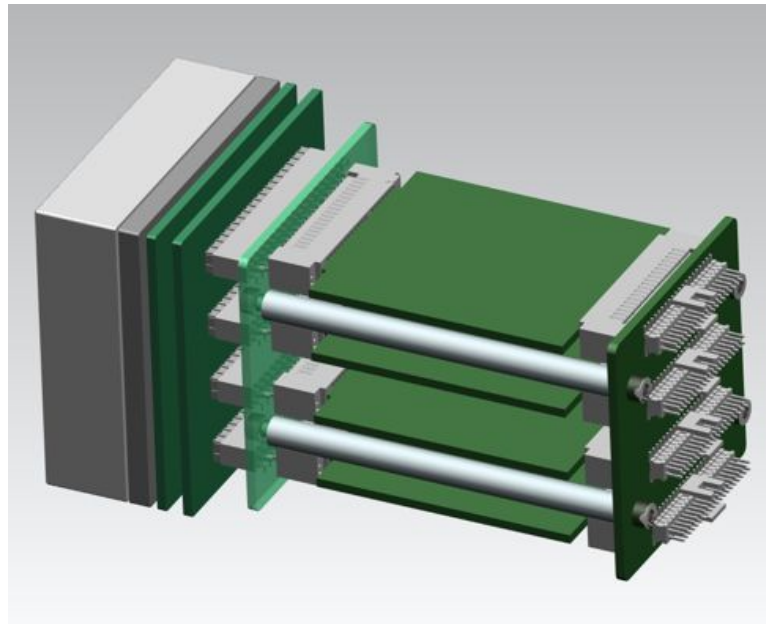


Mechanical Concept

- Amplifiers with edge fingers
- Minimises connector numbers and costs
- 4 boards with 16 amps each (64 channels per detector)
- Modular (with end boards) for detector and flex interfaces.
- If real estate is needed (not currently envisaged), mezzanine boards will be added between



Interface Specification

- Draft Target Module interface specification written and circulated (SLAC)
- Basic input pulse parameters agreed:-
 - 70 Ohm system (Max SLAC can achieve, reduces power consumption, increases available peak pulse voltage)
 - Peak pulse into Target, 1.0V, positive going, capacitively coupled
 - 1.2V under consideration to improve Target signal-noise function
 - Nominal FWHM pulse width 4-9nS
 - Supply nominally 5.0V single ended, and probably <10mA per channel (3.2W per MAPMT) – Amplifier dependant
 - 5.2V under consideration if 1.2V peak pulse required (common mode and rail consideration)
 - Power supply noise immunity tests for SLAC PSU design, still to be done on recently built candidate amplifiers

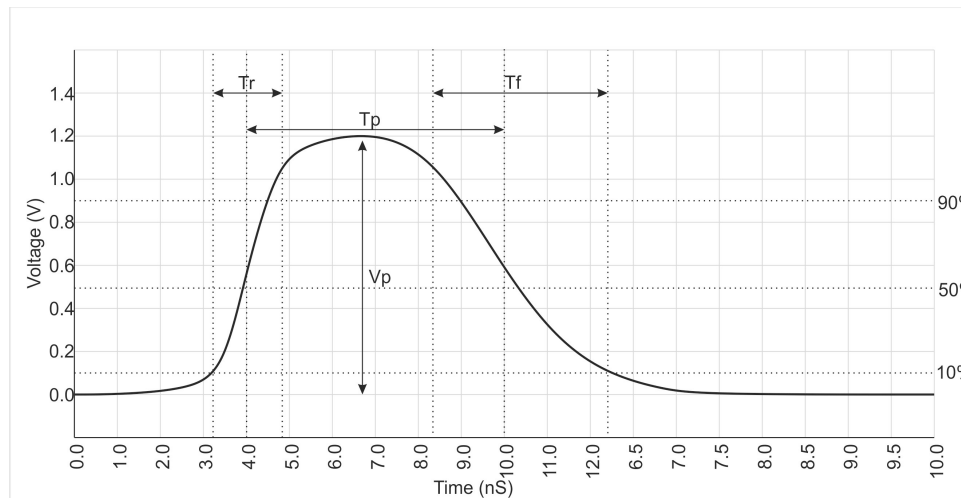

Nominal Pulse Specification (From Monte Carlo)

Candidate amplifiers



- Majority of candidates are current feedback (CFB) types, which is our preferred topology,
 - Currently testing AD8014, OPA2683 and AD8004
- Also looking at quad-core (also known as H-Bridge core) voltage-feedback (VFB) types as these may also have an adequate gain vs bandwidth suitable for this application.
 - Currently AD8038
- Current Feedback has constraints compared to voltage feedback
 - higher offset voltages
 - Higher bias currents,
 - Differing impedances on the inverting and non-inverting inputs,
 - Restricted feedback arrangements,
 - Instability due to stray capacitances.
- However we favour the low inverting input impedance and if we utilise the trans-impedance route (i.e. current to voltage conversion):-
 - lower input voltage noise per given bandwidth,
 - faster slew rates
 - lower distortion.
- We are particularly attracted by extra fast complimentary bipolar (XFCB) devices at this stage
 - e.g ADA4817-2 (first candidate being tested, but has high quiescent current which SLAC were not keen on for PSU design) .

Testing

- Two amplifier systems recently built, being tested, results are promising
- Looking closely at common mode voltage restrictions to ensure batches of amplifiers / PCB build will all behave correctly
- Designs need minor modifications based on results
- Noise immunity needs urgent attention for SLAC PSU design



Initial Test Setup

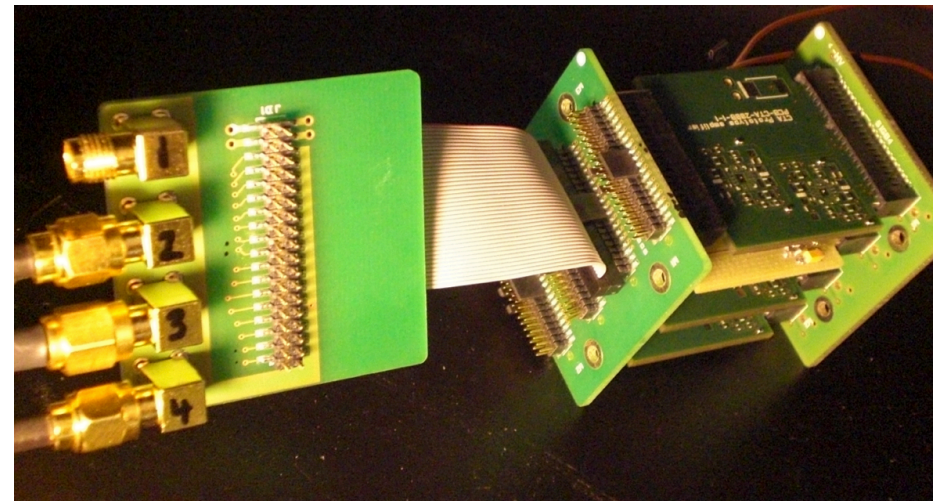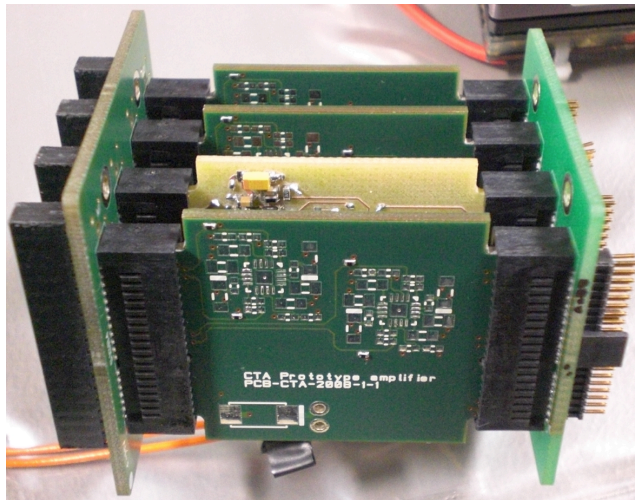- Aim: examine the pulse shape and output range.
- Prototype preamplifier boards connected into MAPM prototype module.
- All channels other MAPM channels terminated with 1K Ohm.
- 4 preamp channels terminated after amplification with 75 Ohm and input with high-Z to the scope.
- MAPM illuminated as described in Mark's talk tomorrow.




Circuit A

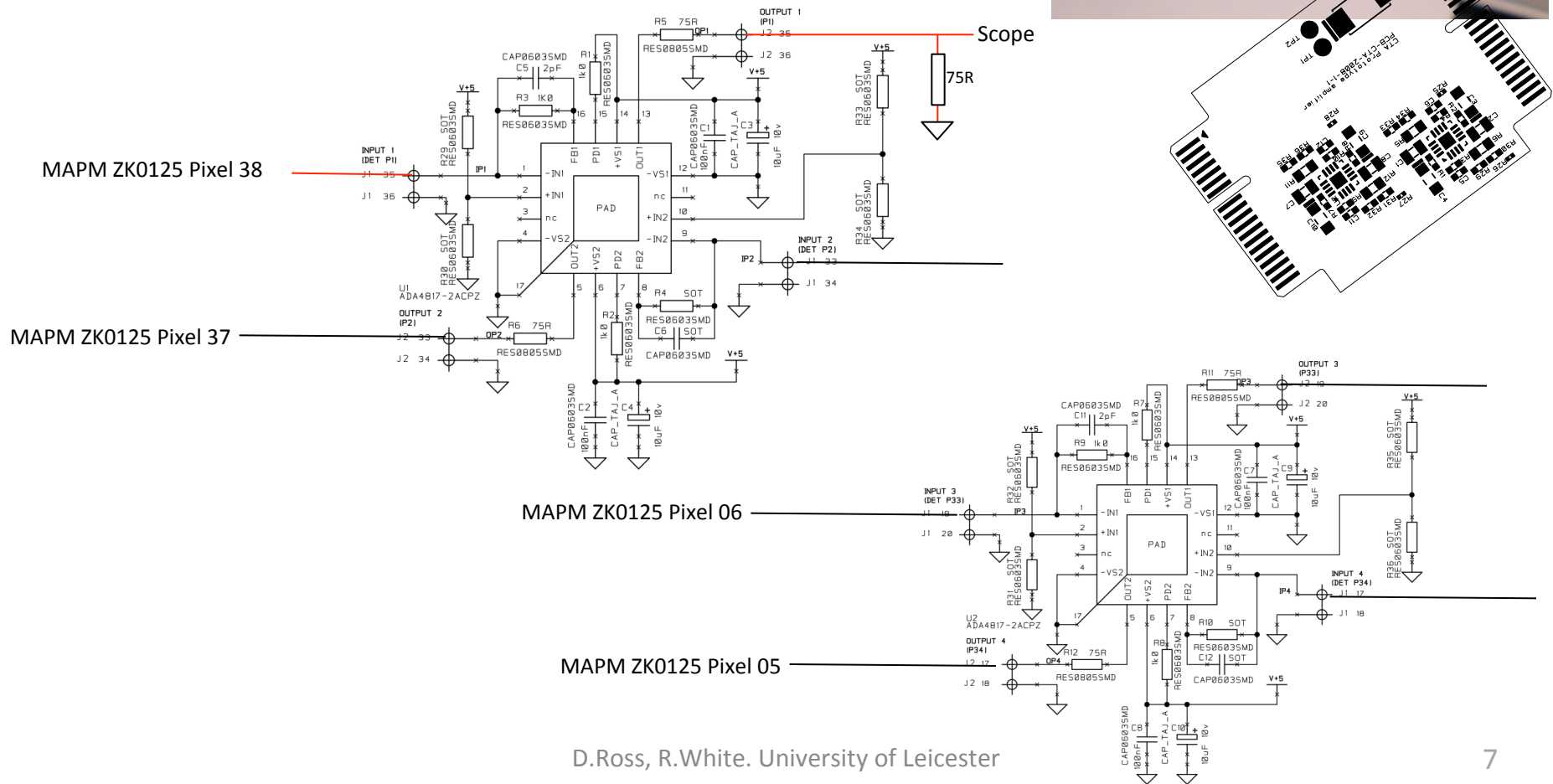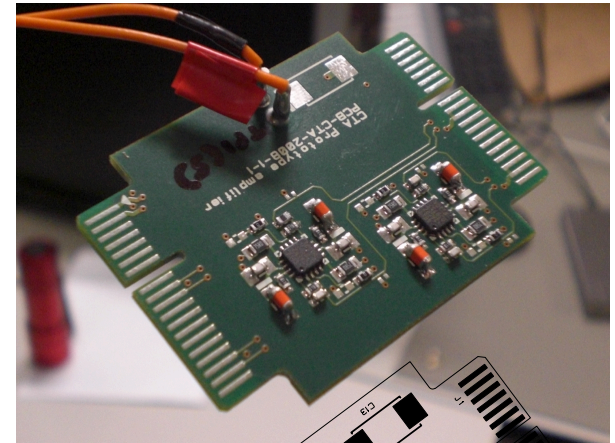- 2 x ADA4817 dual channel
- Pixel 37 investigated in more detail
- ~50 mA @ 5V consumption for all 4 channels



Circuit A: DC Offsets

- ~ 200 mV

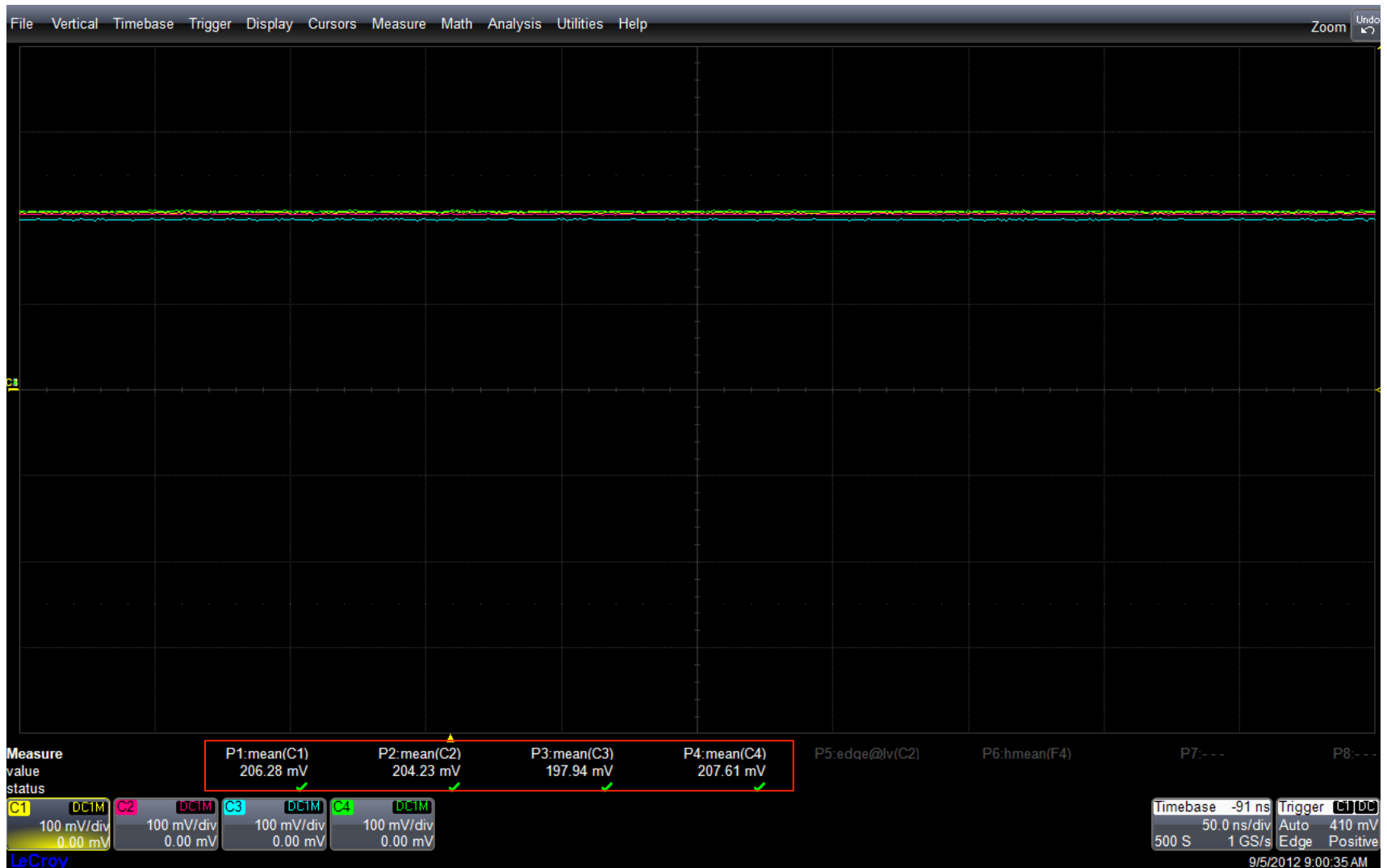


Circuit A: Pulse Shape

Rise Time: ~ 5 ns


Fall Time: ~ 17 ns

FWMH: 8.5 ns

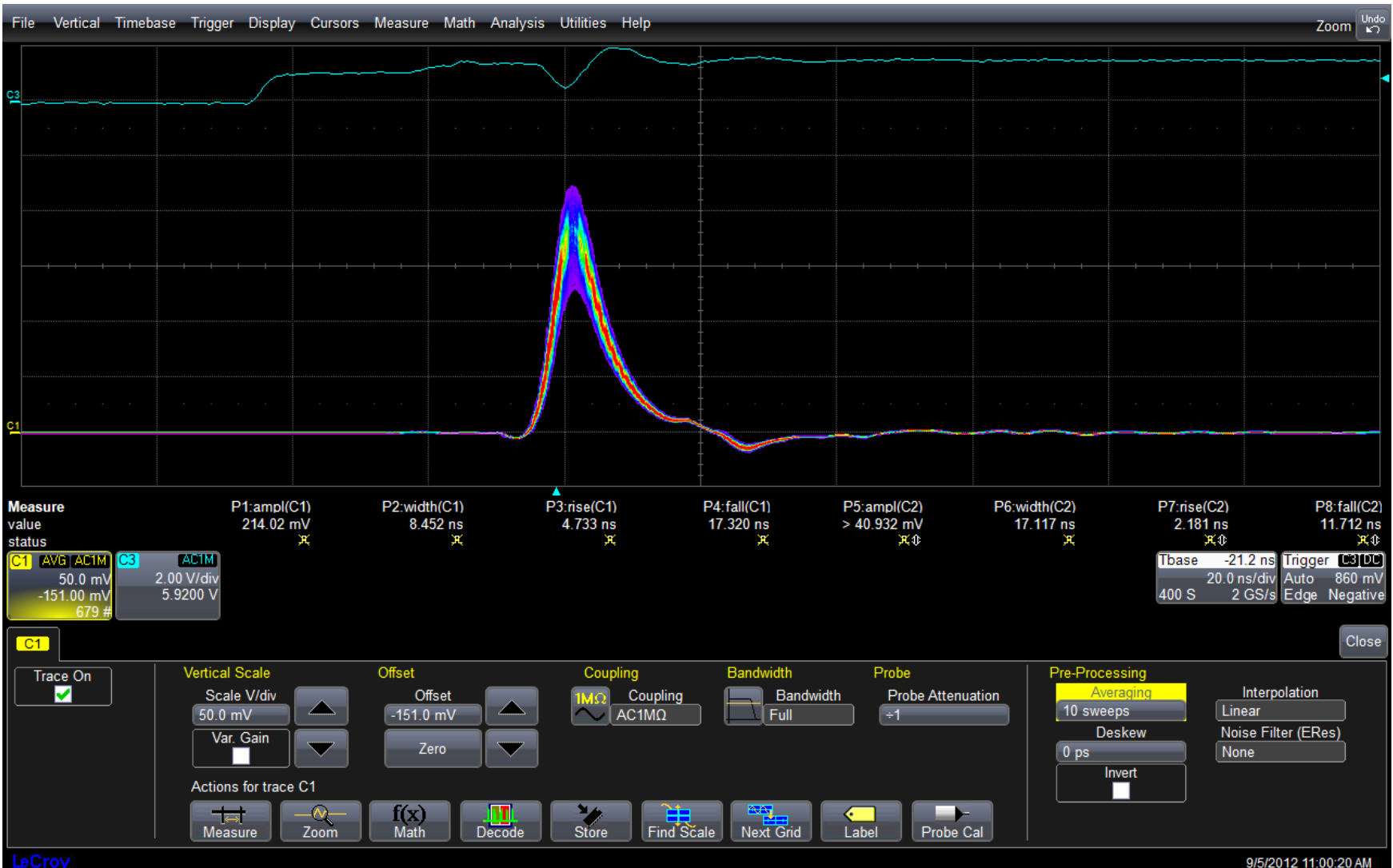


Circuit A: Minimum Signal

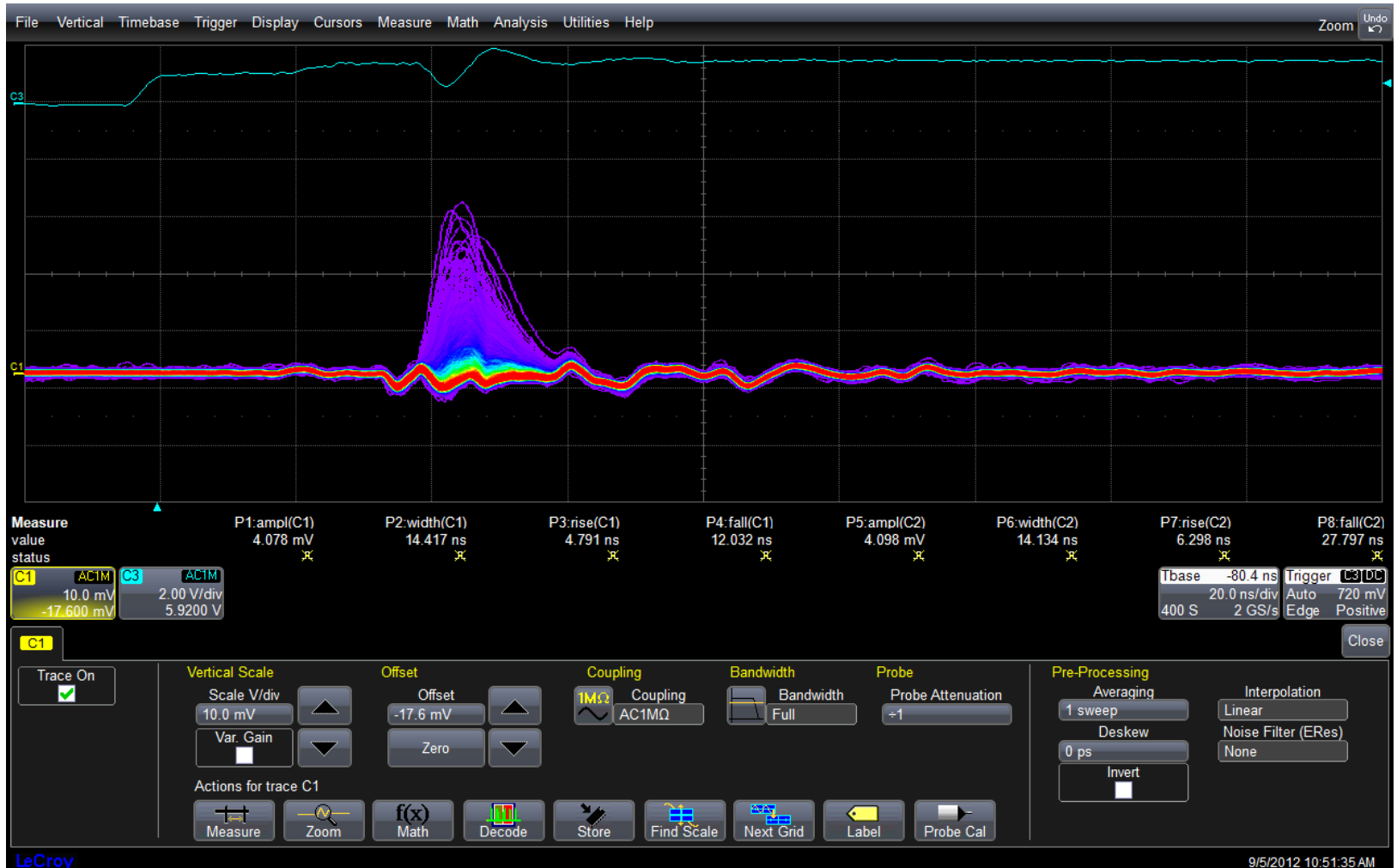- Single p.e. is not resolvable
- Minimum signal is ~ 10 mV




Circuit A: Minimum Signal

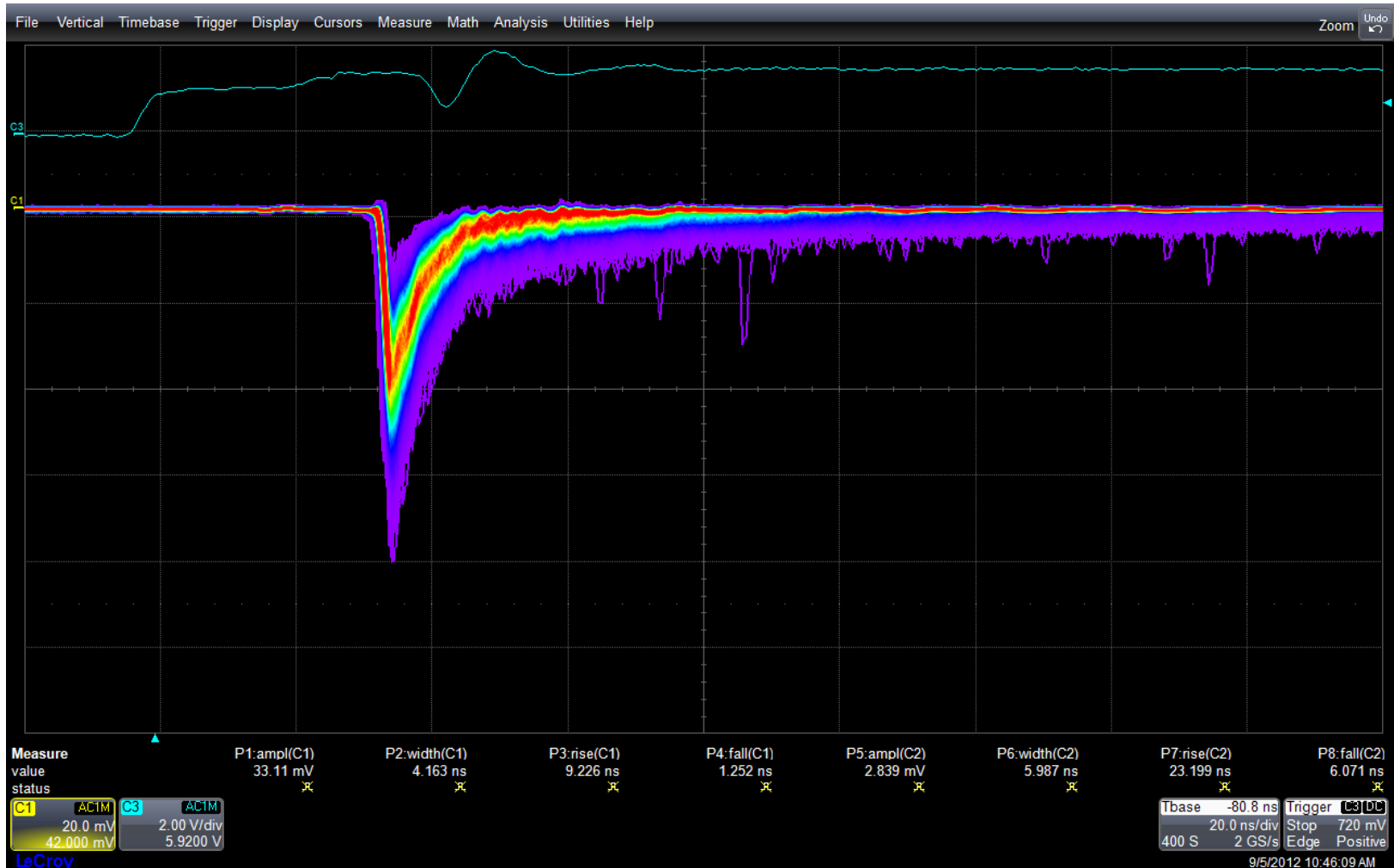- Removing the preamp, this amount of light produces a ~ 40 mV signal.
- By increasing the filter, fitting the SPE and extrapolating, this is ~ 45 p.e.




Circuit A: Maximum Signal

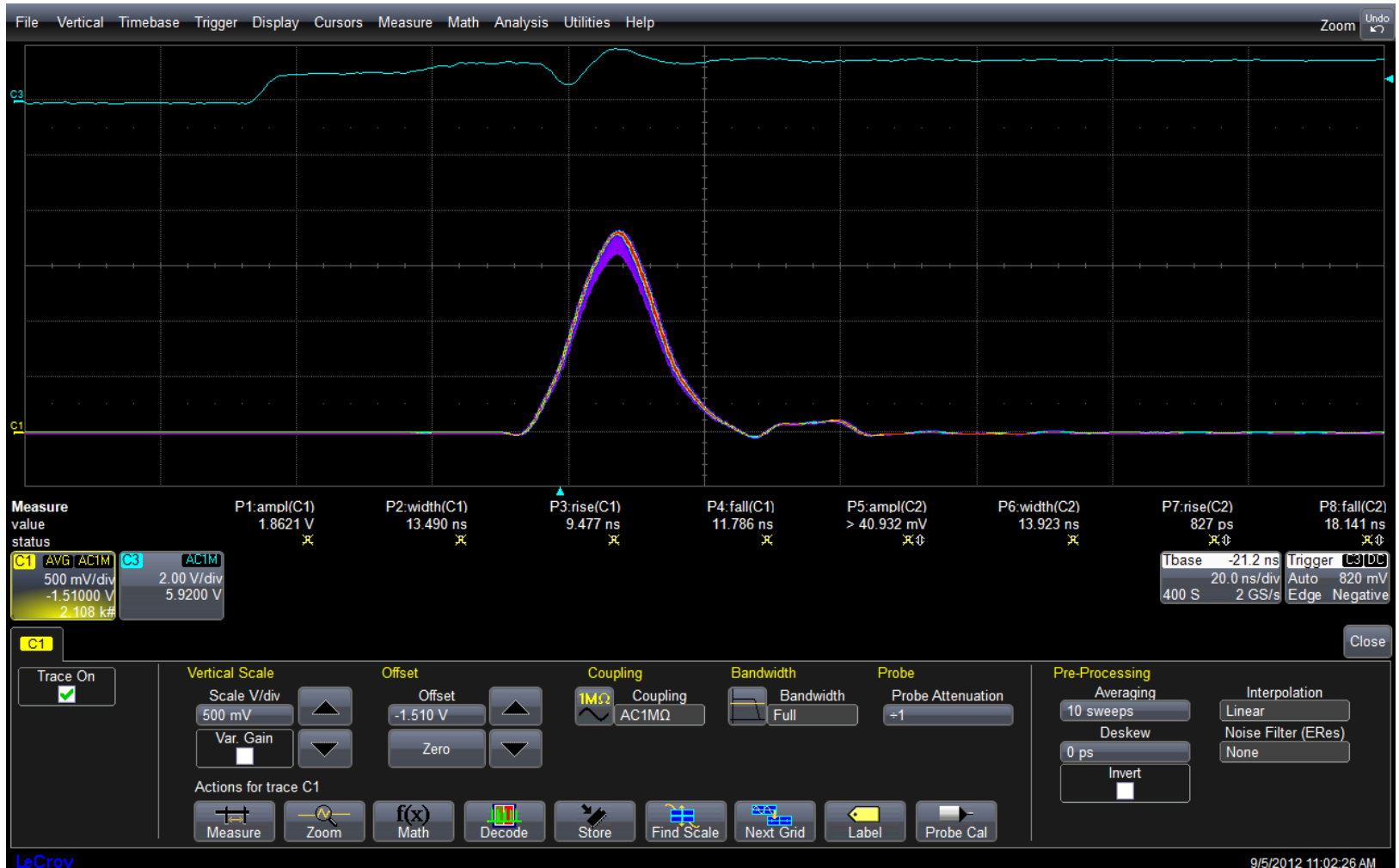- Maximum signal is ~ 1.9 V, very roughly this is ~ 350 p.e.
- Beyond this, the signal saturates.




Circuit B

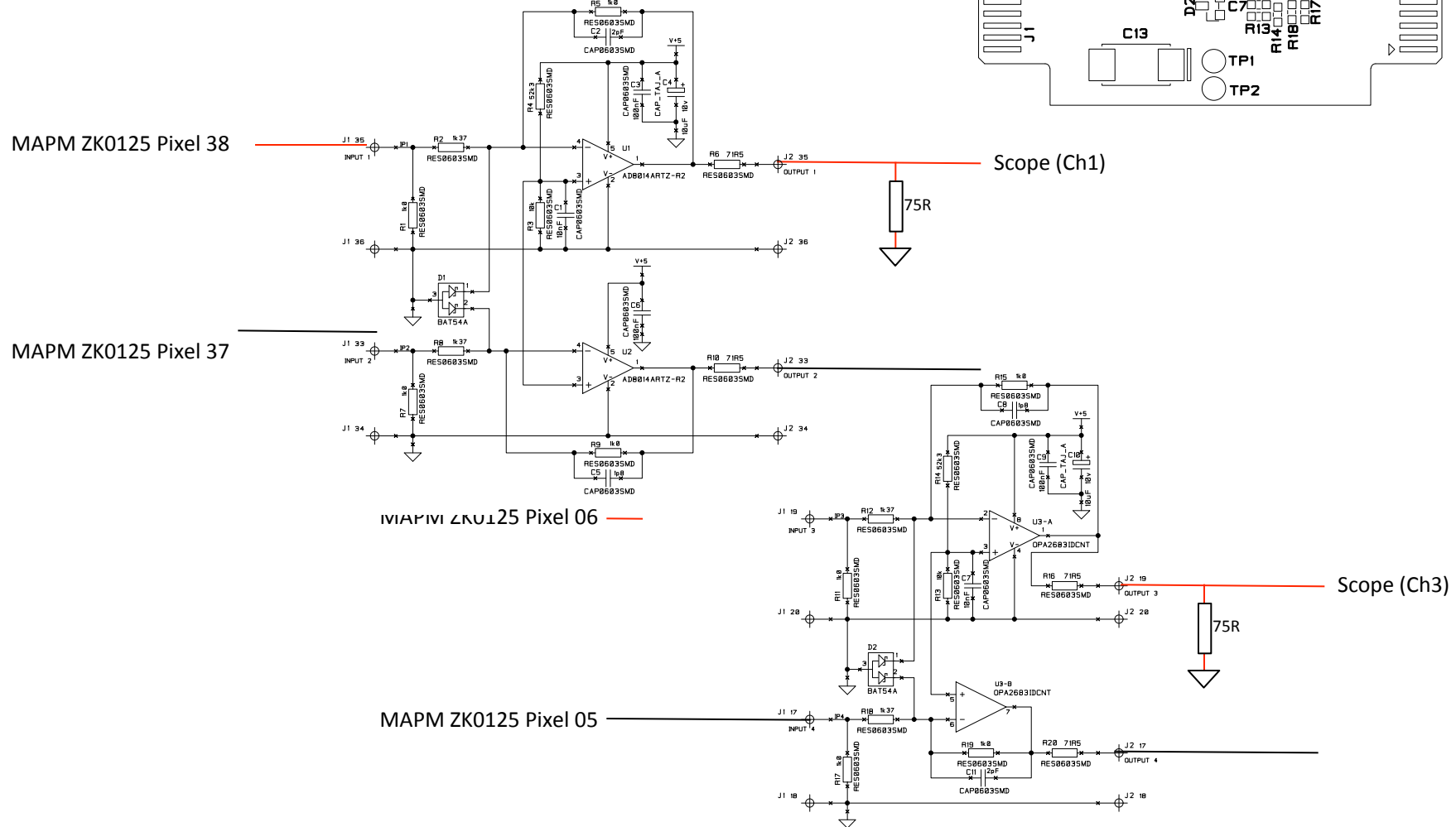- 4 x individual op-amps
- 2 x AD8014, 2 x OPA2683
- Power consumption too low to measure on PSU (<10 mA)



Circuit B: DC Offsets

- AD8014 ~ 670 mV, OPA2683 ~ 635 mV

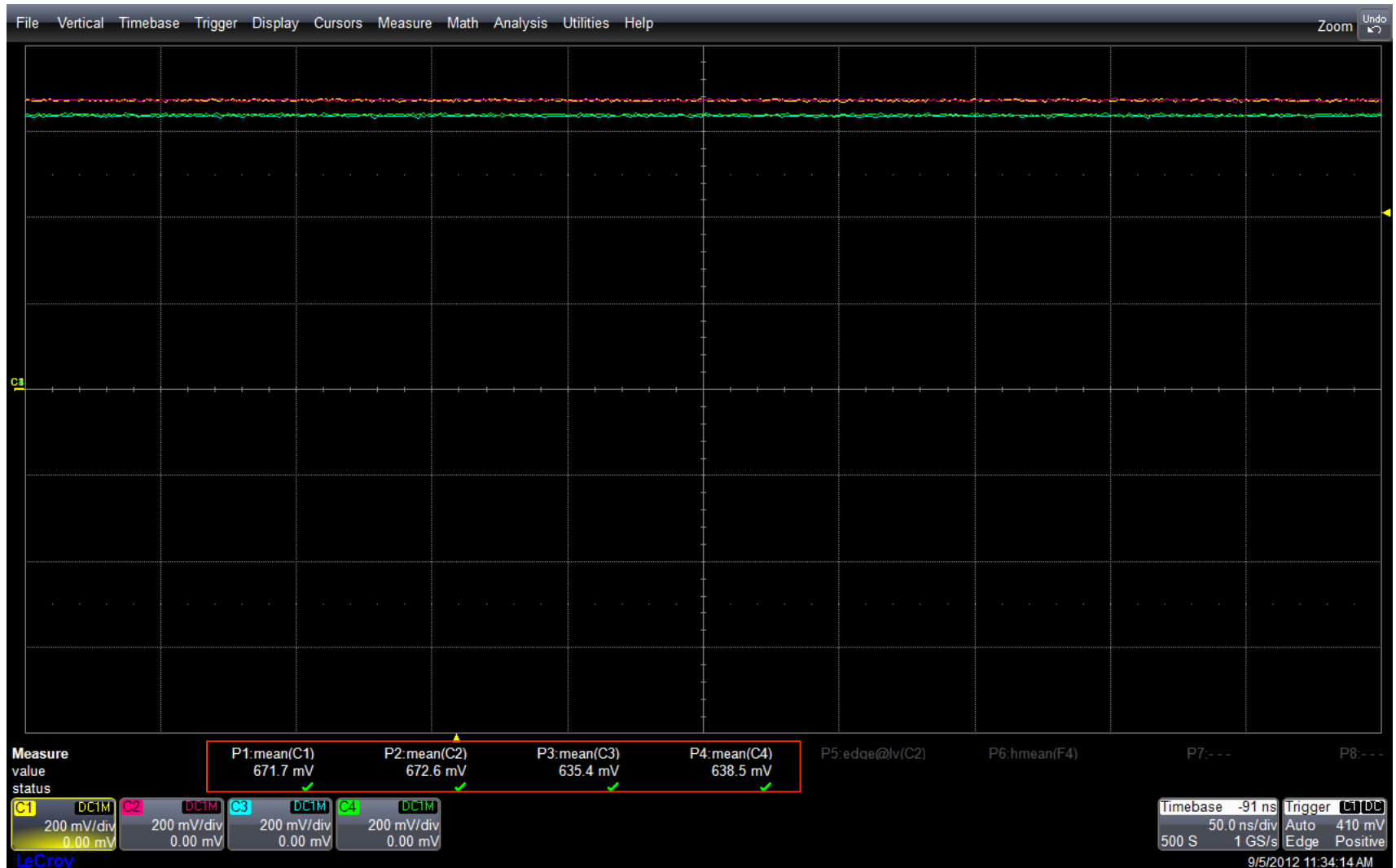


Circuit B: AD8014 Pulse Shape

Rise Time: ~ 5.5 ns

Fall Time: ~ 14.5 ns

FWMH: 19 ns

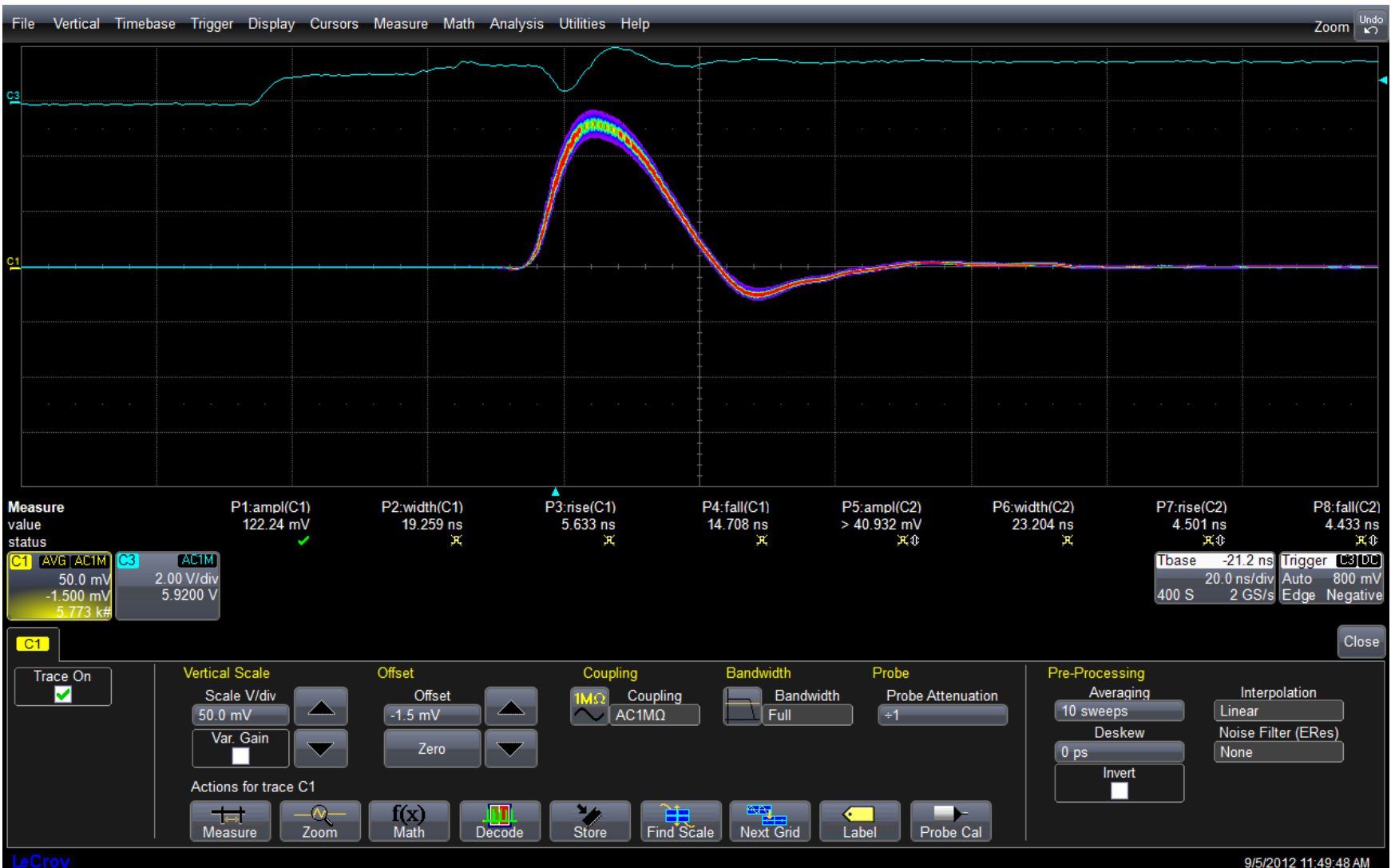


Circuit B: OPA2683 Pulse Shape

Rise Time: ~ 6.5 ns

Fall Time: ~ 20 ns


FWMH: 13 ns

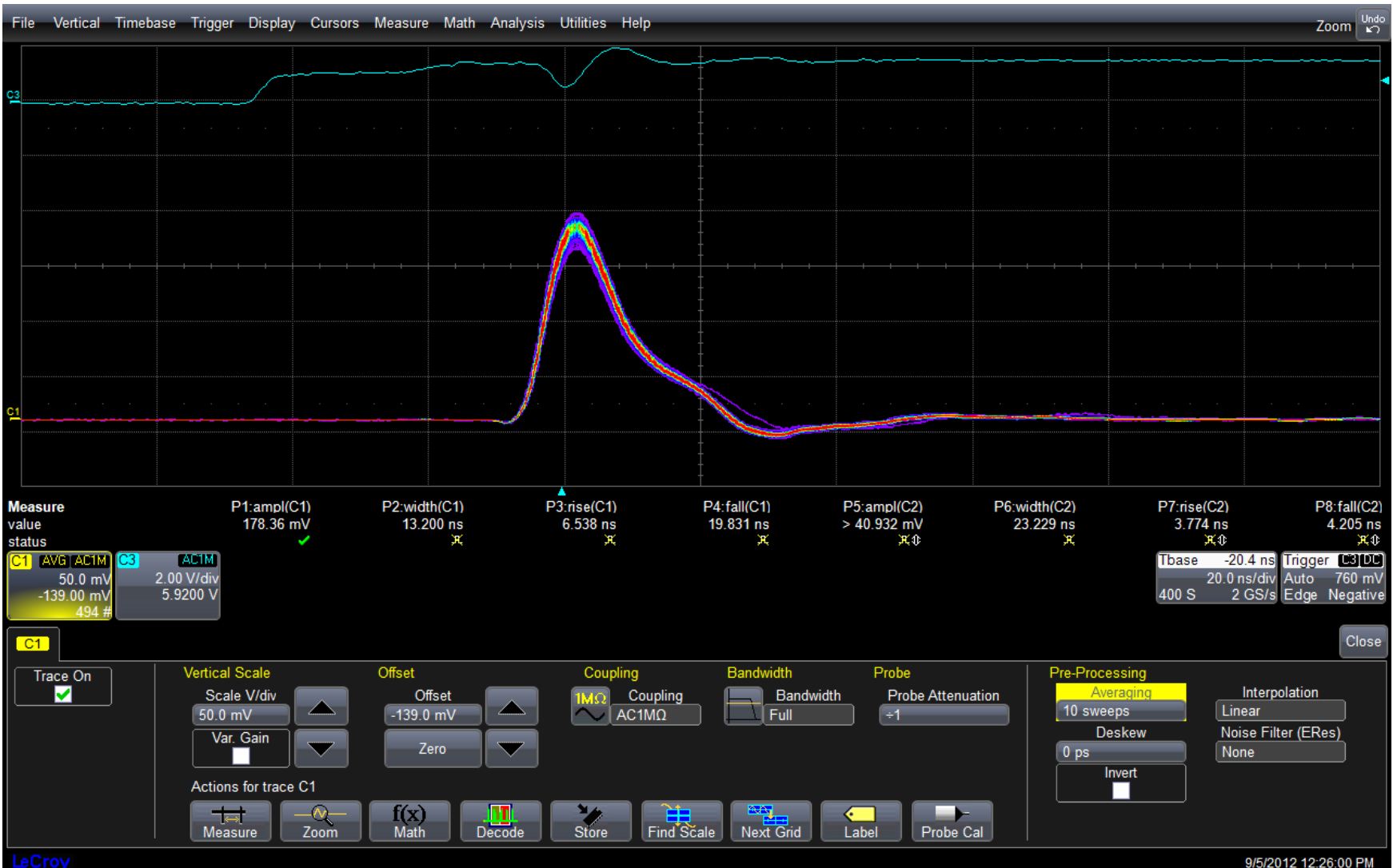


Circuit B: AD8014 Minimum Signal

- Single p.e. is resolvable

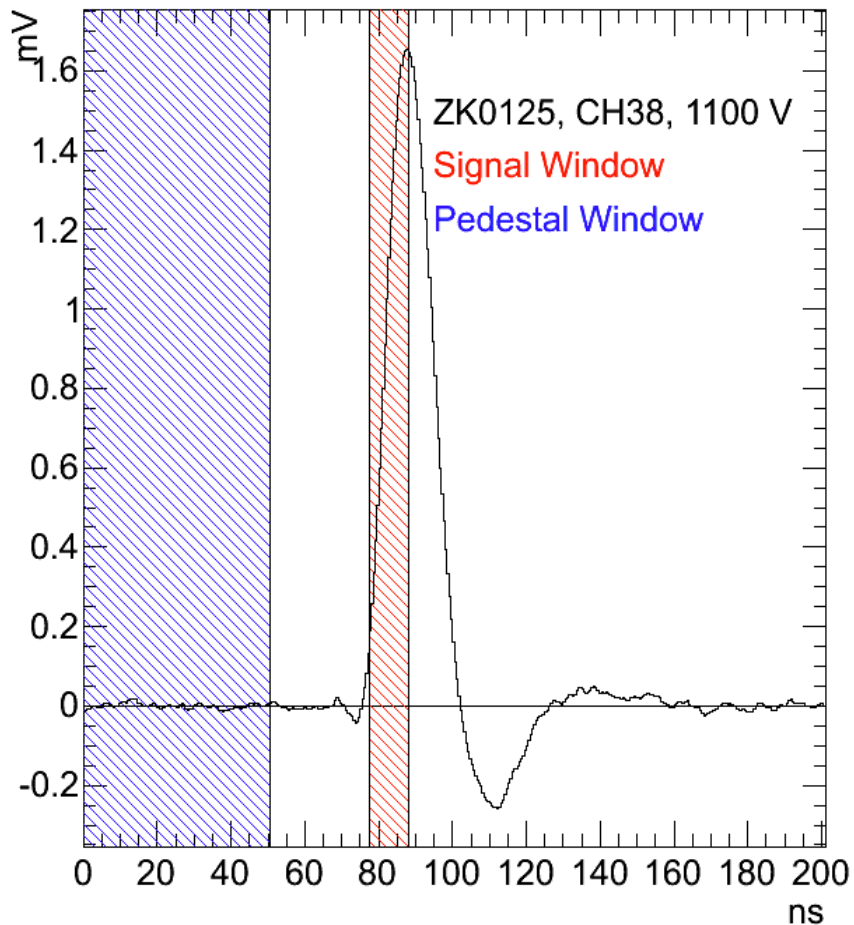Baseline & Pedestal Subtracted Average Signal




Pulse Integral Distribution

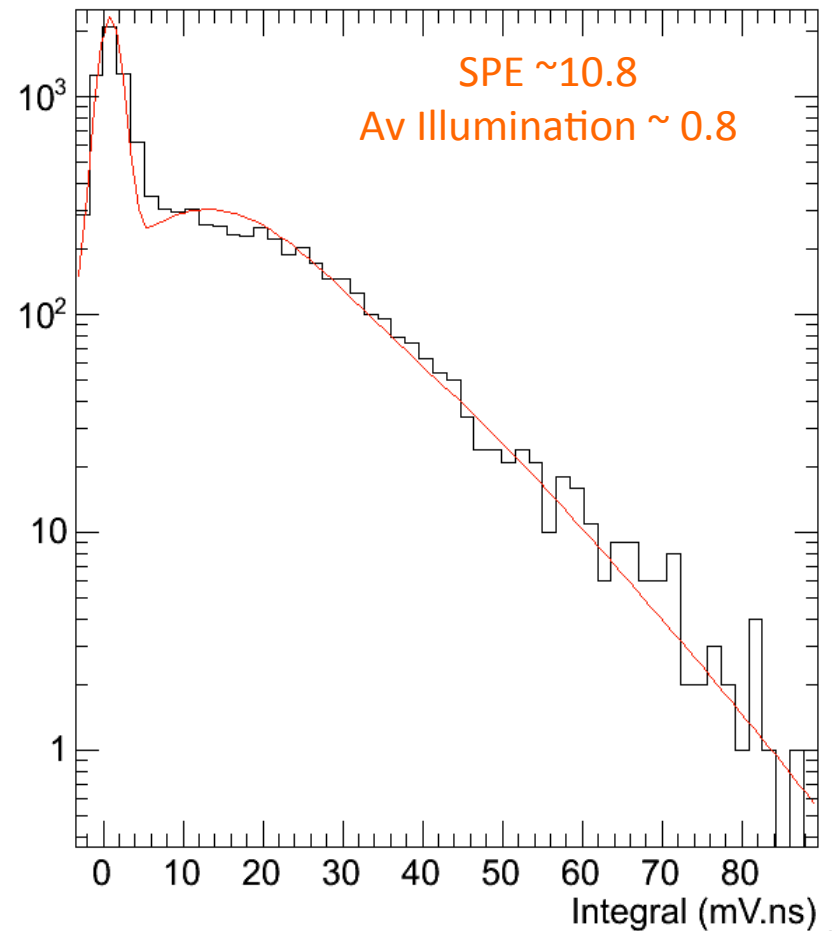


Circuit B: OPA2683 Minimum Signal

- Single p.e. is resolvable

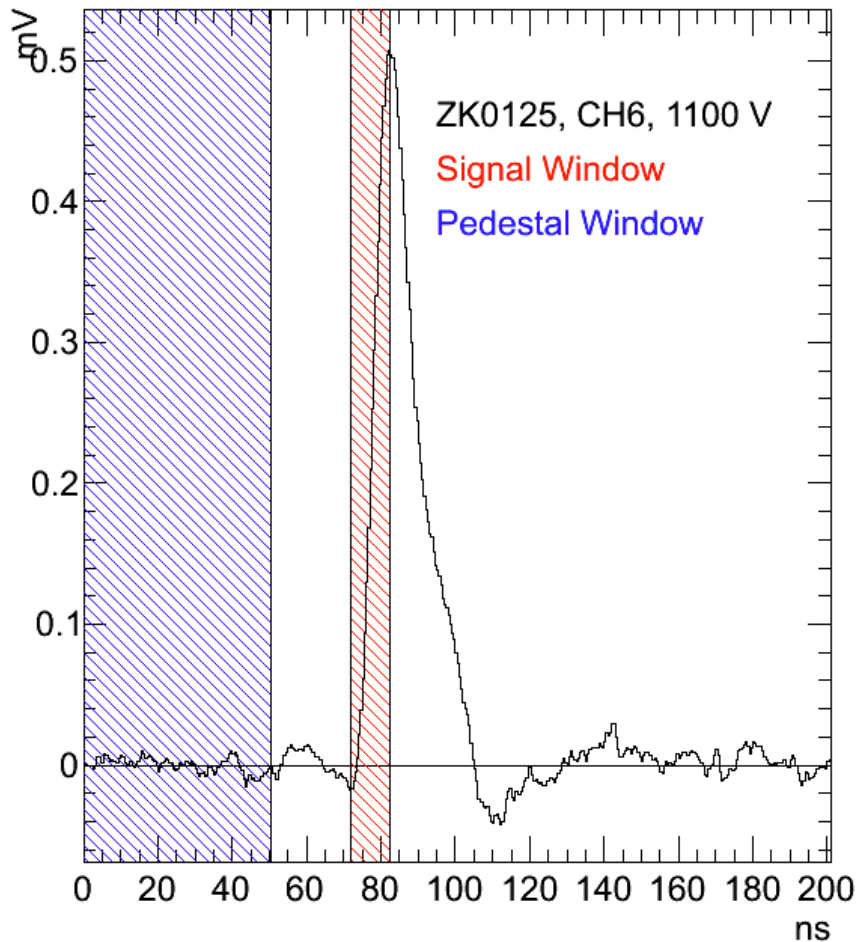Baseline & Pedestal Subtracted Average Signal




Pulse Integral Distribution

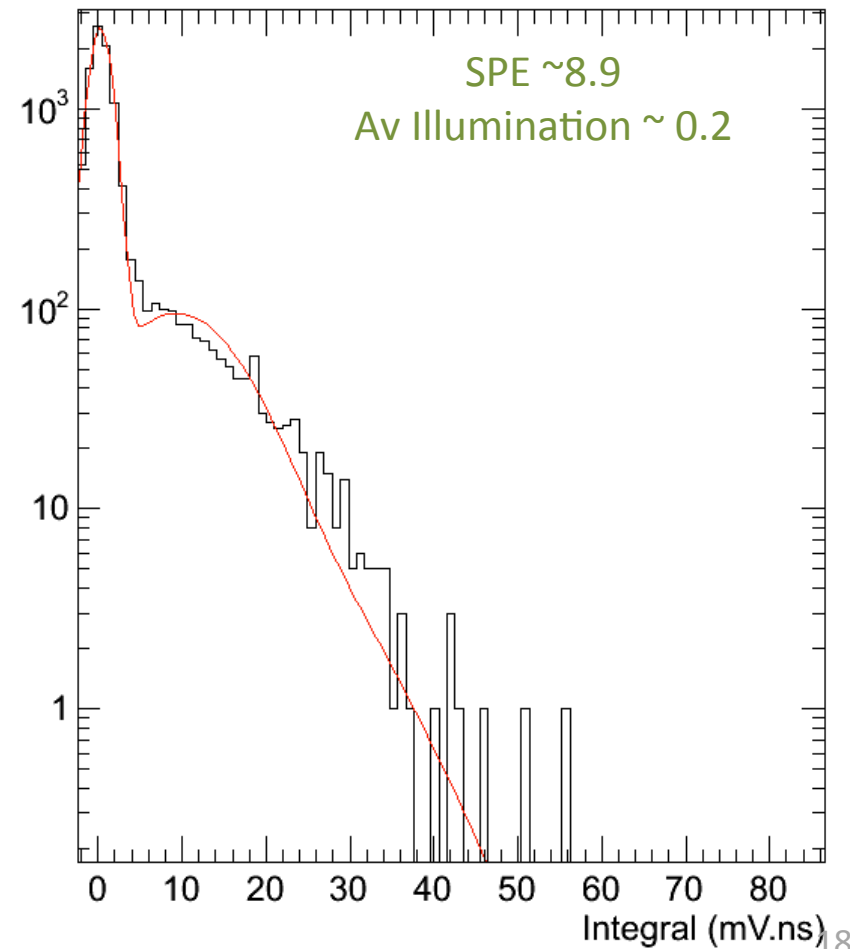


Circuit B: Maximum Signal

AD8014 ~1.5 V (~550 p.e.)

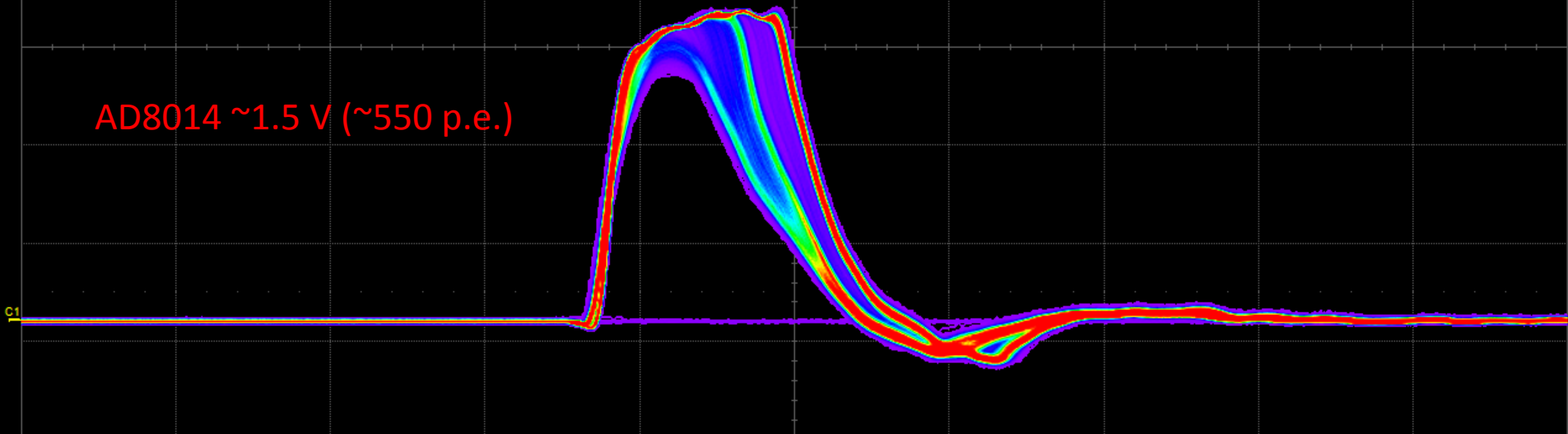

Measure	P1:ampl(C1)	P2:width(C1)	P3:rise(C1)	P4:fall(C1)	P5:ampl(C2)	P6:width(C2)	P7:rise(C2)	P8:fall(C2)
value	1.5467 V	26.429 ns	4.656 ns	10.719 ns	> 40.932 mV	36.957 ns	2.907 ns	22.916 ns
status	✓	✓	✓	✓	✗⬇	✗	✗⬇	✗⬇

OPA2683 ~1.3 V (~850 p.e.)

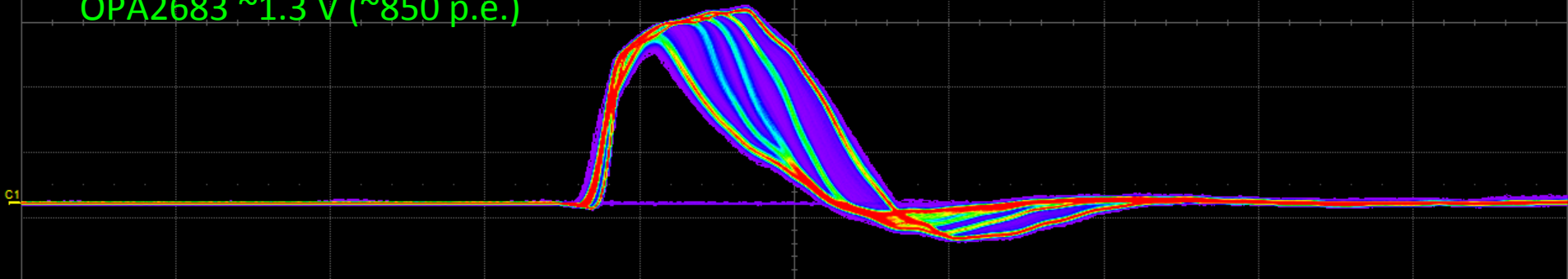

Measure	P1:ampl(C1)	P2:width(C1)	P3:rise(C1)	P4:fall(C1)	P5:ampl(C2)	P6:width(C2)	P7:rise(C2)	P8:fall(C2)
value	1.2677 V	29.230 ns	5.647 ns	17.218 ns	> 40.932 mV	2.457 ns	< 400 ps	< 417 ps
status	✓	✗	✗	✗	✗⬇	✗	✗⬇	✗⬇



C1 ACTIM **C3** ACTIM
500 mV/div 2.00 V/div
-1.39000 V 5.9200 V

Tbase -20.4 ns Trigger **C1** **C3**
20.0 ns/div Stop 760 mV
400 S 2 GS/s Edge Negative

Summary

	T_R (ns)	T_F (ns)	FWHM (ns)	Min (pe) (mV)	Max (pe) (V)
Circuit A: ADA4817	5	17	8.5	45 (10)	350 (1.9)
Circuit B: AD8014	5.5	14.5	19	0.8 (1.6)	550 (1.5)
Circuit B: OPA2683	6.5	20	13	0.2 (0.5)	850 (1.3)

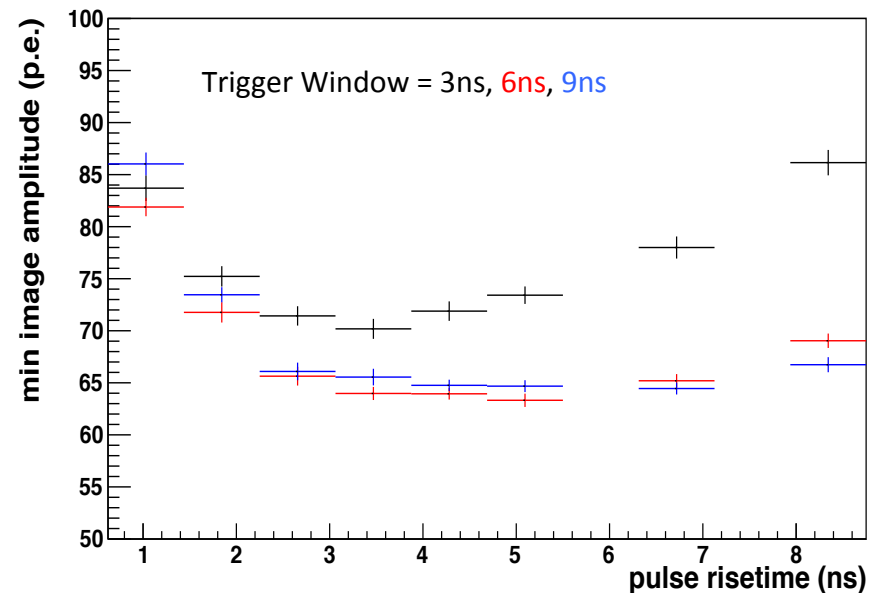
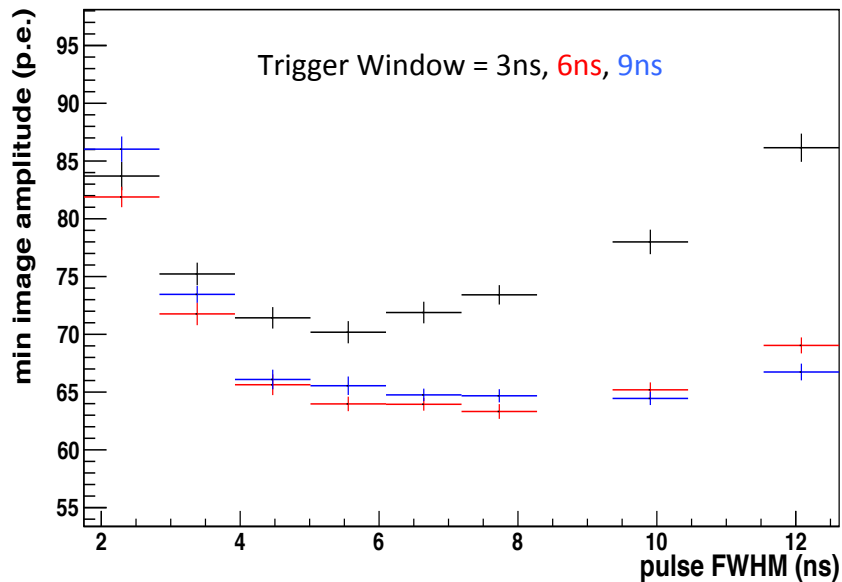
- Initial tests look very good!
- Shaping can be altered based on these results as can output range.
- Can compare the pulse shape to Stefan's simulations:



Summary

	T_R (ns)	T_F (ns)	FWHM (ns)	Min (pe) (mV)	Max (pe) (V)
Circuit A: ADA4817	5	17	8.5	45 (10)	350 (1.9)
Circuit B: AD8014	5.5	14.5	19	0.8 (1.6)	550 (1.5)
Circuit B: OPA2683	6.5	20	13	0.2 (0.5)	850 (1.3)

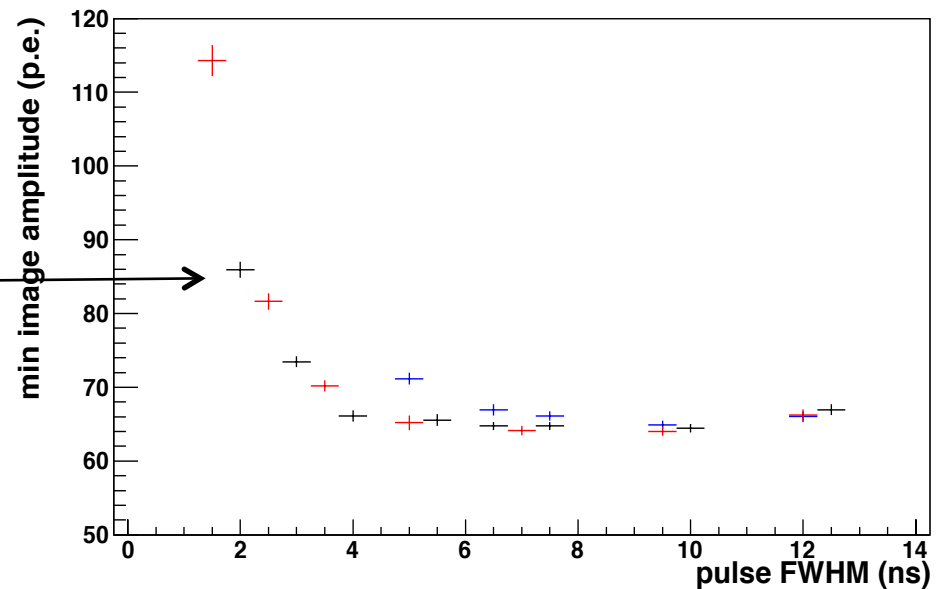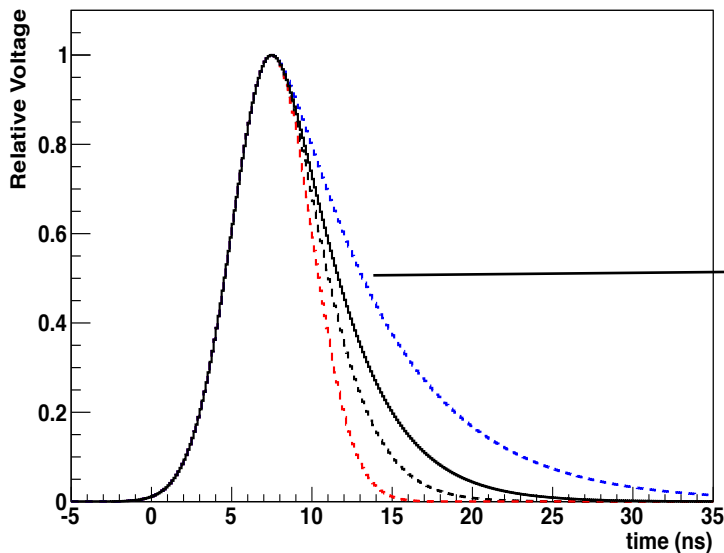- Initial tests look very good!
- Shaping can be altered based on these results as can output range.
- Can compare the pulse shape to Stefan's simulations:



Further Considerations

- MAPMT or SiPMT ? – different amplifier designs but same principle ?
- CHEC thermal impact of different amplifier power consumptions?
- Different mechanical solutions, dependant on detector configuration ?